

## Dynamic Circuit Analysis


$$e(t) = V_R(t) + V_L(t) + V_C(t)$$

$$V_R(t) = Ri(t)$$

$$V_L(t) = L \frac{di(t)}{dt}$$

$$i_C(t) = C \frac{dV_C(t)}{dt} \rightarrow V_C(t) = \frac{1}{C} \int_0^t i_C(t) dt + V_C(0)$$
 
$$e(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i_C(t) dt + V_C(0)$$



$$\frac{de(t)}{dt} = L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t)$$

State equation:  $\dot{x}(t) = f(x, t)$        $\dot{x}(t) = \frac{dx(t)}{dt}$

State variable:  $x(t)$

$$x_1(t) \equiv i(t) \qquad x_2(t) \equiv \frac{di(t)}{dt}$$


$$\dot{x}_1(t) = x_2(t) \qquad \dot{x}_2(t) = \frac{d^2 i(t)}{dt^2}$$

$$\underbrace{\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix}}_{\underline{\dot{x}}(t)} = \underbrace{\begin{bmatrix} 0 & 1 \\ -1/LC & -R/L \end{bmatrix}}_A \underbrace{\begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}}_{\underline{x}(t)} + \underbrace{\begin{bmatrix} 0 \\ 1/L \end{bmatrix}}_{B_1} \dot{e}(t)$$

In general case:  $\underline{\dot{x}}(t) = A\underline{x}(t) + B\underline{e}(t) + B_1\dot{\underline{e}}(t)$

*Assumption:*

 
There is no loop which consists of only capacitors and independent voltage sources and there is no cut set which consists of only inductors and independent current sources.



Analysis method:

- 1) Pick a tree of the digraph of the circuit which includes all the capacitors and voltage sources. Inductors and current sources will be links.  
→ proper tree
- 2) The twig capacitor voltages and the link inductor currents are chosen as state variables.
- 3) For each fundamental cut set defined by the twig capacitor, write KCL equations.
- 4) For each fundamental loop defined by the link inductor, write KVL equations.

 *Example 9.1* Obtain state equations of the circuit given in the figure.




## Output equation

y: currents or voltages of other elements in the circuit

$$\dot{\underline{x}}(t) = A\underline{x}(t) + B\underline{e}(t) + B_1\dot{\underline{e}}(t)$$
 
$$\underline{y}(t) = C\underline{x}(t) + D\underline{e}(t) + D_1\dot{\underline{e}}(t)$$



$$y = i_R = [1 \quad 0] \begin{bmatrix} i_L \\ V_C \end{bmatrix}$$


$$y = V_L = -Ri_L - V_C + e(t) = [-R \quad -1] \begin{bmatrix} i_L \\ V_C \end{bmatrix} + e(t)$$

Finding state equations in circuits consisting of RLC and linear multi-ports

1. Capacitors and independent voltage sources will be twigs.
2. Element equations in the element graph are considered if the tree is not complete.

Element voltages will be twigs; element currents will be links.

*Example 9.2*

 

## Solution of State Equations

Order of the circuit = number of state variables in the state equations

### First order circuits

$$\dot{x}(t) = ax(t) + be(t), \quad x(t_0) = x_0 \quad a, b \in \mathbb{R}$$

$$x(t) = \underbrace{e^{a(t-t_0)}x(t_0)}_{\text{zero-input response}} + \underbrace{\int_{t_0}^t e^{-a\tau}be(\tau)d\tau}_{\text{zero-state response}}$$

$$\tau = \frac{1}{a} : \text{time constant}$$



## Definition

1. If zero state response goes to zero for all  $x_0$  as  $t \rightarrow \infty$ , then the circuit is asymptotically stable.
2. If zero state response stays finite for all  $x_0$  as  $t \rightarrow \infty$ , then the circuit is stable.
3. If zero state response goes to infinity for some  $x_0$  as  $t \rightarrow \infty$ , then the circuit is unstable.