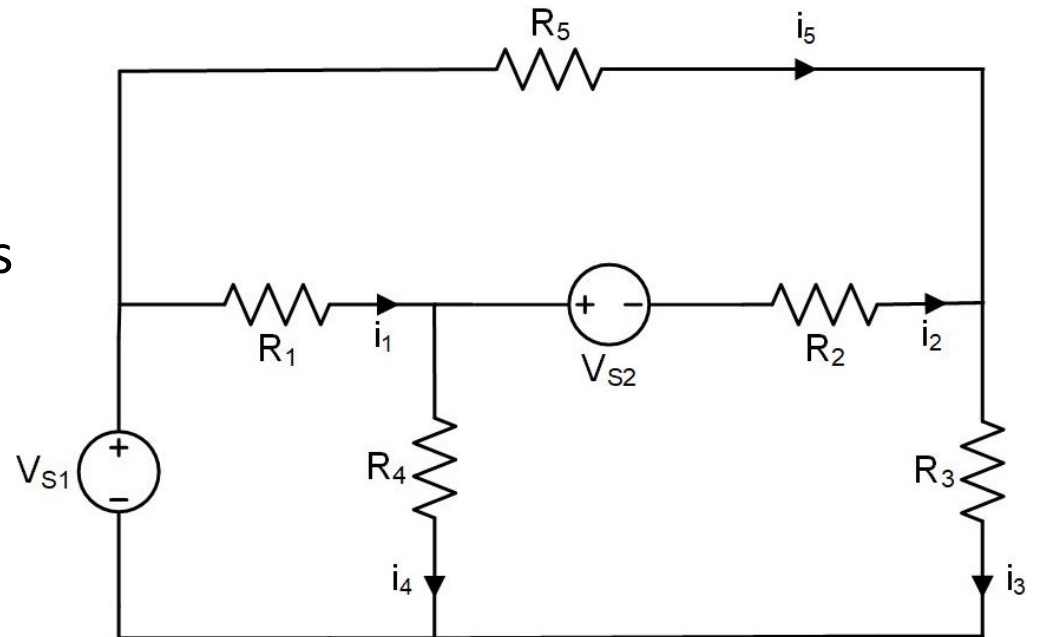


## Mesh Analysis


A mesh is defined as a loop which does not contain any other loops.

Assumption: the elements are i-controlled

1. Write voltage equation in the mesh (KVL)
2. Write element (branch) voltages in terms of element currents
3. Replace element (branch) currents with mesh currents



B

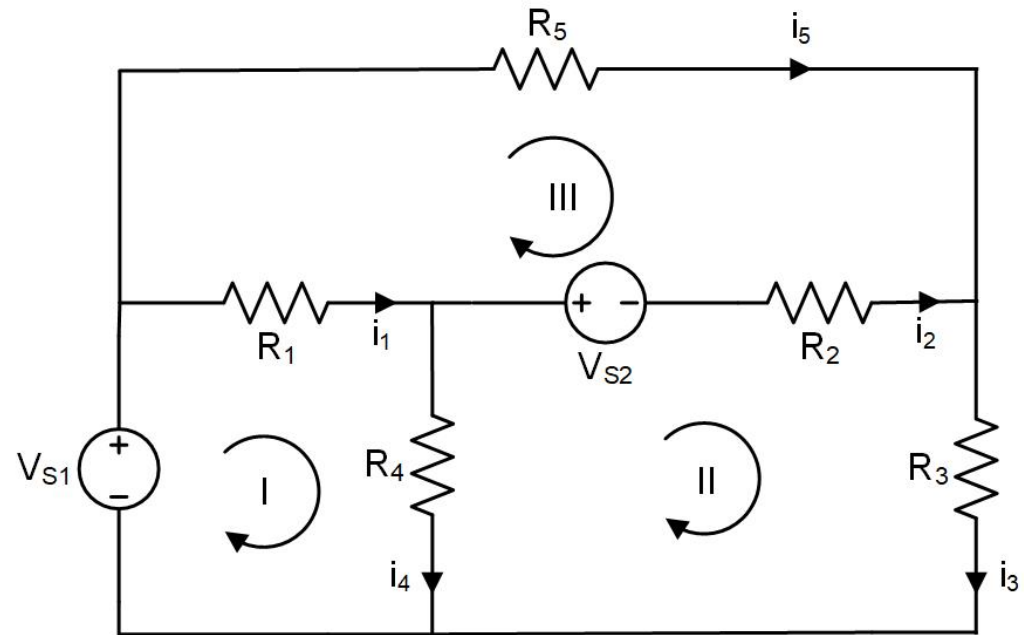

$$\text{I)} \quad V_1 + V_4 - V_{S1} = 0$$

$$\text{II)} \quad V_2 + V_3 - V_4 + V_{S2} = 0$$

$$\text{III)} \quad V_5 - V_2 - V_{S2} - V_1 = 0$$

$$\text{I)} \quad i_1 R_1 + i_4 R_4 = V_{S1}$$

$$\text{II)} \quad i_2 R_2 + \dots = \dots$$

$$\text{III)} \quad -R_1 i_1 - \dots = \dots$$

$$\text{I)} \quad R_1 (I_{m1} - I_{m3}) + R_4 (I_{m1} - I_{m2}) = V_{S1}$$

$$\text{II)} \quad R_2 (I_{m2} - I_{m3}) + \dots = \dots$$

$$\text{III)} \quad -R_1 (I_{m1} - I_{m3}) - \dots = \dots$$

$$\underbrace{\begin{bmatrix} R_1 + R_4 & -R_4 & -R_1 \\ -R_4 & R_2 + R_3 + R_4 & -R_2 \\ -R_1 & -R_2 & R_1 + R_2 + R_5 \end{bmatrix}}_{Z_m} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix} = \begin{bmatrix} V_{S1} \\ -V_{S2} \\ V_{S2} \end{bmatrix}$$

$Z_m$ : mesh impedance matrix

1.  $z_{kk}$  is the sum of impedances of the elements in mesh  $k$ .
2. For  $i \neq j$ ,  $z_{ik} = z_{ki}$  if a circuit consists of two-terminal elements only.
3.  $z_{ik}$  is either the sum or the negative sum of the impedances of elements which are common to the two meshes.  
If in the element common to the two meshes the reference directions of the two meshes are the same  $z_{ik}$  is the sum; otherwise  $z_{ik}$  is the negative sum.

4.  $V_s^k$  is the algebraic sum of voltage sources in the  $k$ th mesh.  
It is positive if the direction of the mesh is opposite to the direction of the voltage source.

### Modified mesh analysis

If there are also elements which are not i-controlled.

1. Write mesh equations using mesh currents as variables.
2. Whenever an element is encountered that is not i-controlled, introduce in the mesh equation the corresponding branch voltage as a new variable.
3. Add the branch equation of that element as a new equation in terms of mesh currents and voltages of the elements which are not i-controlled.

$$\text{I)} \quad (R_1 + R_2)I_{m1} - R_2I_{m2} - R_1I_{m3} + V_{Is} = 0$$

$$\text{II)} \quad -R_2I_{m1} + \dots$$


$$V_d = r i_1 = \dots$$

$$\text{III)} \quad -R_1I_{m1} + \dots$$

Extra equations:

$$I_{m1} = \dots$$

$$i_d = gV_2 = \dots$$

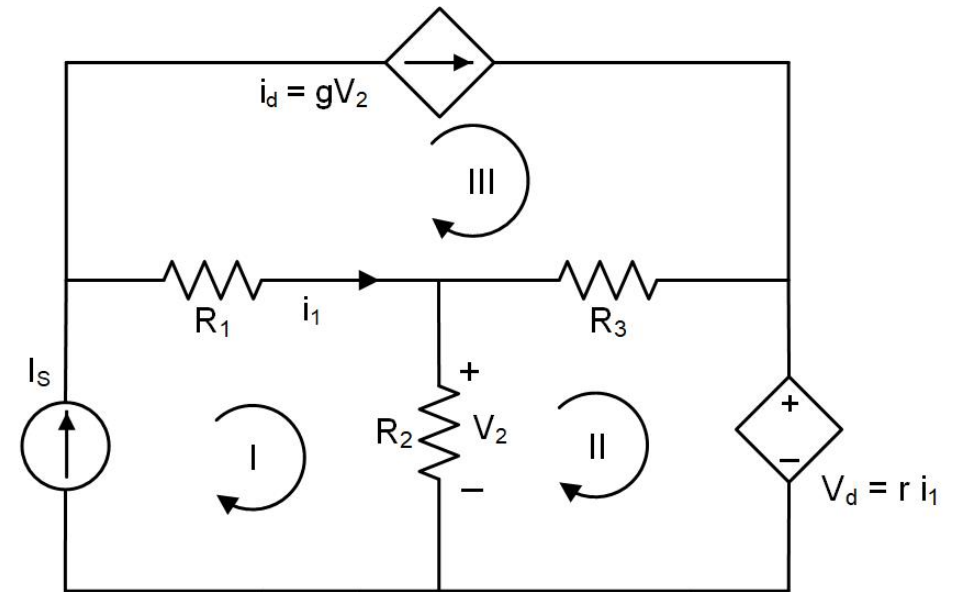

$$\begin{bmatrix} R_1 + R_2 & -R_2 & -R_1 & 1 & 0 \\ r - R_2 & R_2 + R_3 & -R_3 - r & 0 & 0 \\ -R_1 & -R_3 & R_1 + R_3 & 0 & 1 \\ 1 & 0 & 0 & 0 & 0 \\ gR_2 & -gR_2 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \\ V_{ls} \\ V_{id} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ I_s \\ 0 \end{bmatrix}$$