

Rules:

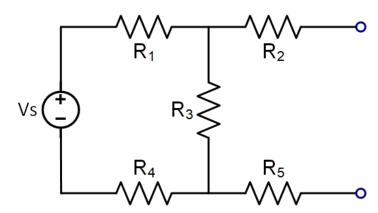- 1) Your homework should be hand-written.
- 2) Don't include a cover page. Use both sides of the paper.
- 3) Have at least 1,5 cm margin from the edges.
- 4) The grades of identical or very similar looking homeworks will be divided to the number of such homeworks.
- 5) Your homeworks will be collected in the class on Wednesdays before the first lecture, till 12:30. If you bring your homework between 12:31 13:30 your grade will be multiplied with 0,7. After 13:30 no homework will be accepted.
- 6) You must sign on a sheet of paper as proof of handing in.
 If you want to hand in your homework before Wednesday, you must contact research assistant Görkem Yazgaç (Office: 8301).
- 1) Find the Norton equivalent of the one-port given below. (100 points) $(Vs = 71V, R_1 = 1\Omega, R_2 = 2\Omega, R_3 = 3\Omega, R_4 = 4\Omega, R_5 = 5\Omega)$



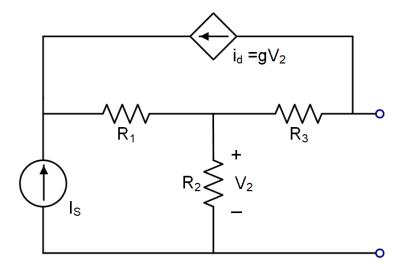2) Find the Thevenin equivalent of the one-port given below. (100 points) $(I_S = 6A, R_1 = 1\Omega, R_2 = \frac{1}{2}\Omega, R_3 = \frac{1}{3}\Omega, g = 4S)$



Deadline of the 6th HW is 11 April 2018 12:30.