

HOMWORK 5

TEVFIK OZGU

150180082

1. Analyze the synchronous sequential circuit given in the figure below by answering following questions.

- Determine the input functions of the flip-flops.

Input Functions Of J-K Flip Flop:

$$J = \bar{X}Q_1$$

$$K = \overline{X \oplus Q_1} = \overline{(\bar{X}Q_1 + X\bar{Q}_1)} = (\bar{X} + Q_1)(X + \bar{Q}_1) = \bar{Q}_1\bar{X} + XQ_1$$

Input Functions of D Flip Flop:

$$D = X$$

- Determine the next states (use Q0 for JK-FF, and Q1 for D-FF) and output expression.

$$Q_0^+ = J\bar{Q}_0 + \bar{K}Q_0 \longrightarrow Q_0^+ = \bar{X}Q_1\bar{Q}_0 + \overline{(\bar{X}Q_1 + X\bar{Q}_1)}Q_0$$

$$Q_0^+ = \bar{X}Q_1\bar{Q}_0 + (\bar{X}Q_1 + X\bar{Q}_1)Q_0 = \bar{X}Q_1\bar{Q}_0 + \bar{X}Q_1Q_0 + X\bar{Q}_1Q_0$$

$$Q_0^+ = \bar{X}Q_1\bar{Q}_0 + \bar{X}Q_1Q_0 + X\bar{Q}_1Q_0 = \bar{X}Q_1(\bar{Q}_0 + Q_0) + X\bar{Q}_1Q_0 \quad (\text{Inverse})$$

$$Q_0^+ = \bar{X}Q_1 + X\bar{Q}_1Q_0 \quad (\text{Next State of J-K flip flop})$$

$$Q_1^+ = D \longrightarrow Q_1^+ = X \quad (\text{Next State of D flip flop})$$

$$Z = XQ_0Q_1 \quad (\text{Output Expression})$$

- Derive the state/output table.

$Q_1^+ Q_0^+ Z \diagdown X$		0		1	
		$Q_1 Q_0$			
00		00,0		10,0	
01		00,0		11,0	
10		01,0		10,0	
11		01,0		10,1	

To make the table more understandable we assign state names to state codes.

00:A


01:B

10:C

11:D

$Q_1^+ Q_0^+ Z$		X	
$Q_1 Q_0$		0	1
A		A,0	C,0
B		A,0	D,0
C		B,0	C,0
D		B,0	C,1

- Draw the state transition diagram.

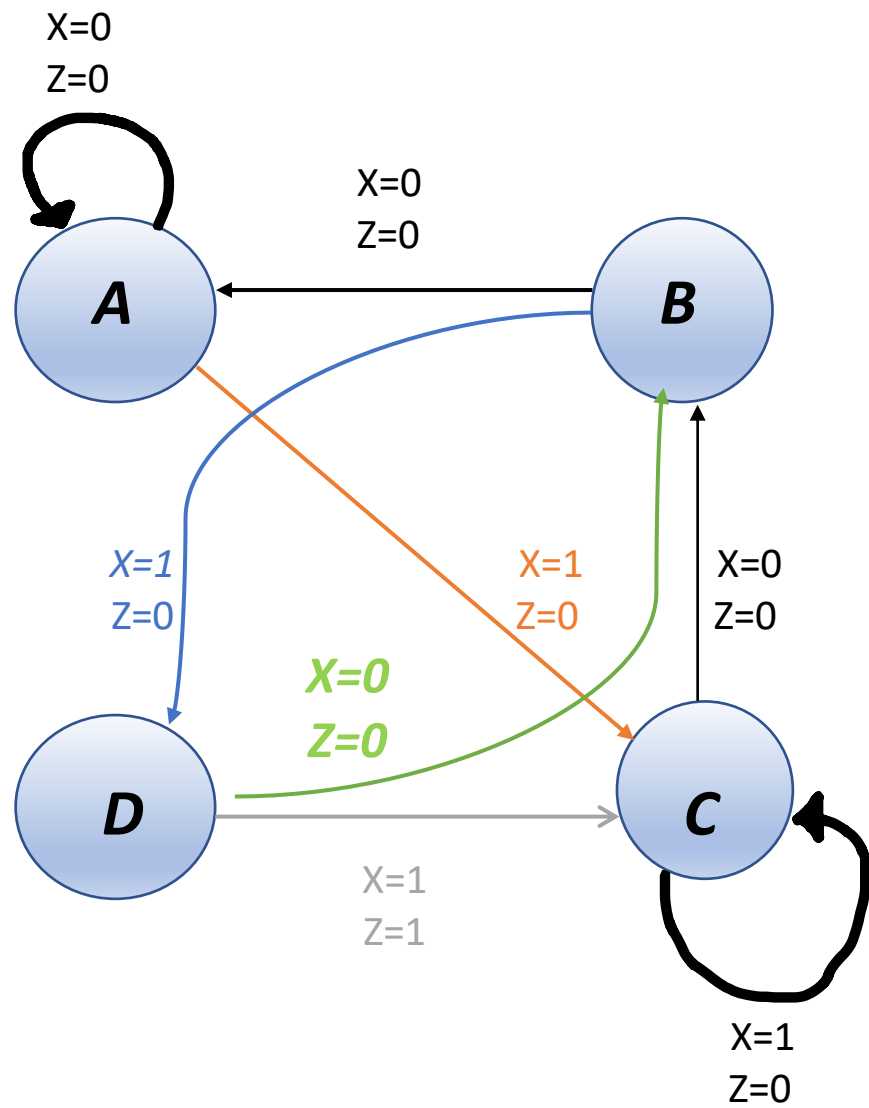

2. Assume that the machine is in state 00 and the output is also 0. Write the shortest possible sequence of X (consecutive values of X) that makes the output 1.

- I. Initially machine is in state 00 so machine is in A state.
- II. If X=1 is given new state is c and output is 0.
- III. Then we give X=0 so new state is B and output is 0.
- IV. Then we give X=1 so machine is In state D and output is 0.
- V. Finally, we give X=1 so machine is in state C and output is 1.

Sequence of X: $1 \rightarrow 0 \rightarrow 1 \rightarrow 1$