
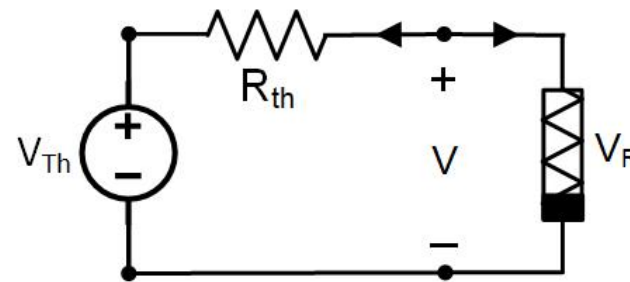



Nonlinear Circuits

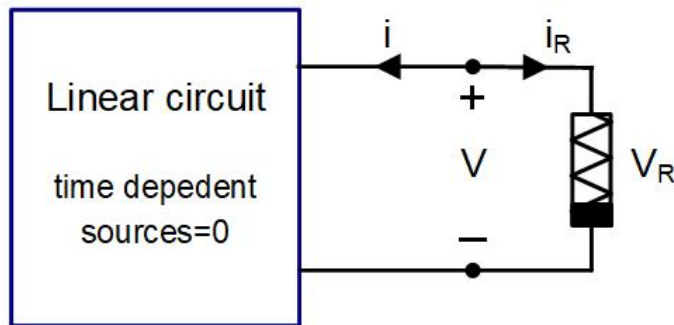Operating point The solution (I_Q , V_Q) found when time dependent sources are suppressed in the circuit.




$$V_R = f(i_R) \quad V = V_R \quad i + i_R = 0$$

$$V_{th} - R_{th}i - V_R = 0 \rightarrow V_R = -R_{th}i_R + V_{th}$$

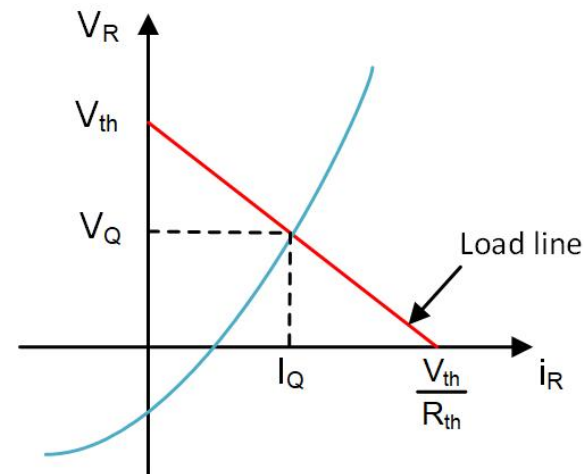

Example 8.1

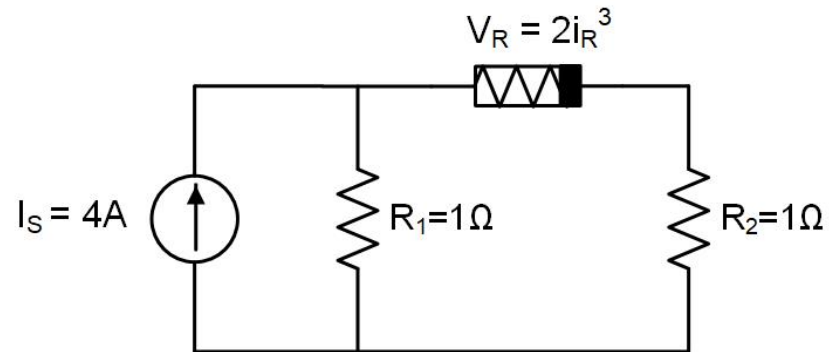




Small signal analysis

$$V_s = V_0 + e(t)$$

$$e(t) = E \cos(\omega t)$$

$$|E| \ll |V_0| \text{ for all the time}$$

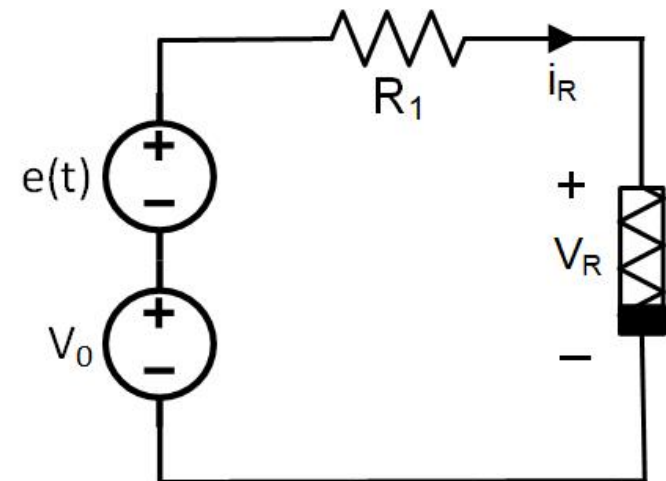

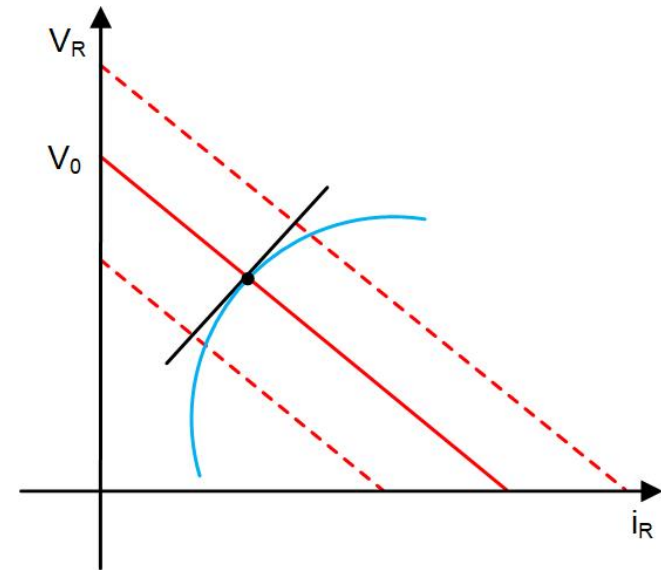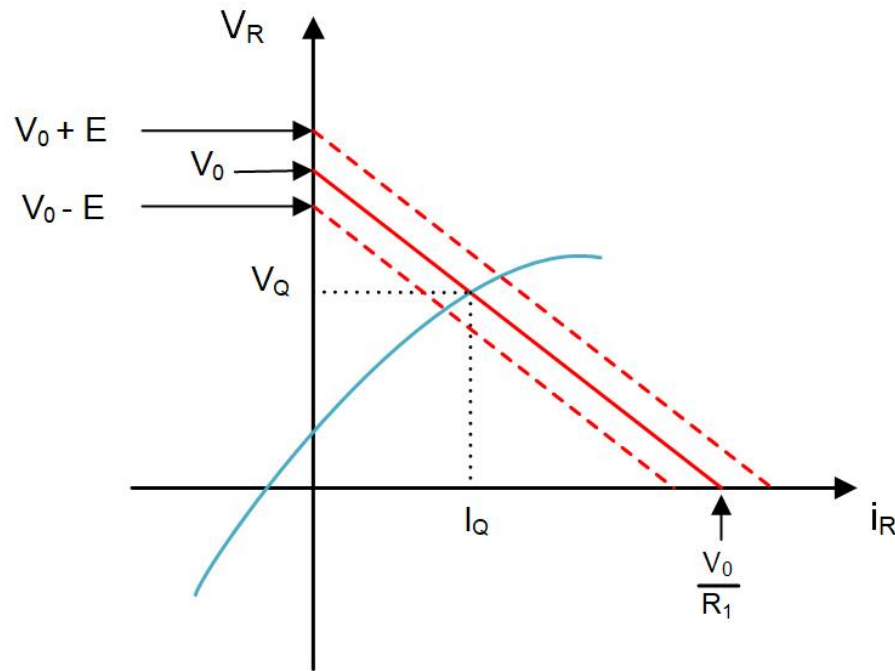

1. Time dependent sources are suppressed. Operating point (I_Q, V_Q) is found.
2. Nonlinear elements are linearized around their operating points. Small signal equivalents are found.

$$V_R(t) - V_{R_Q} = f'(I_{R_Q}) (i_R(t) - I_{R_Q})$$

$$\left. \begin{aligned} \widetilde{i}_R(t) &= i_R(t) - I_{R_Q} \\ \widetilde{V}_R(t) &= V_R(t) - V_{R_Q} \end{aligned} \right\} \text{Small signal components}$$

$$\widetilde{V}_R(t) = f'(I_{R_Q}) \widetilde{i}_R(t)$$

$f'(I_{R_Q})$: small signal equivalent of the nonlinear element at the operating point Q ($f'(I_{R_Q}) = R_Q$)


3. Time independent sources are suppressed. Small signal components $(\widetilde{V}_R(t), \widetilde{i}_R(t))$ are found.

$$4. V_R(t) \cong V_Q + \widetilde{V}_R(t) \qquad i_R(t) \cong I_Q + \widetilde{i}_R(t)$$

Example 8.2

$$e(t) = 0,5 \sin(1000t)$$

$$V_R = i_R^3 - 6i_R^2 + 9i_R$$

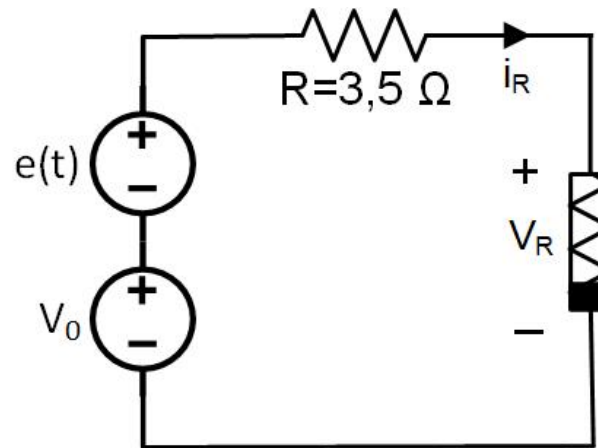

Small signal model of nonlinear multi-terminal elements

$n+1$ terminal element $\rightarrow \mathbf{y}, \mathbf{x}$

$$y_1 = f_1(x_1, x_2, \dots, x_n)$$

$$y_2 = f_2(x_1, x_2, \dots, x_n)$$

$$\vdots \qquad \qquad \vdots$$

$$y_n = f_n(x_1, x_2, \dots, x_n)$$

Small signal model around (x_Q, y_Q)

$$y_1 - y_{1Q} = \frac{\partial f_1}{\partial x_1} (x_1 - x_{1Q}) + \frac{\partial f_1}{\partial x_2} (x_2 - x_{2Q}) + \cdots + \frac{\partial f_1}{\partial x_n} (x_n - x_{nQ})$$

$$y_2 - y_{2Q} = \frac{\partial f_2}{\partial x_1} (x_1 - x_{1Q}) + \frac{\partial f_2}{\partial x_2} (x_2 - x_{2Q}) + \cdots + \frac{\partial f_2}{\partial x_n} (x_n - x_{nQ})$$

$$\vdots$$
$$\vdots$$

$$y_n - y_{nQ} = \frac{\partial f_n}{\partial x_1} (x_1 - x_{1Q}) + \frac{\partial f_n}{\partial x_2} (x_2 - x_{2Q}) + \cdots + \frac{\partial f_n}{\partial x_n} (x_n - x_{nQ})$$

$$\frac{\partial f}{\partial x} = J = \begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} & \cdots & \frac{\partial f_1}{\partial x_n} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} & \cdots & \frac{\partial f_2}{\partial x_n} \\ \vdots & \vdots & & \vdots \\ \frac{\partial f_n}{\partial x_1} & \frac{\partial f_n}{\partial x_2} & \cdots & \frac{\partial f_n}{\partial x_n} \end{bmatrix}$$

$$J_{ij} = \frac{\partial f_i}{\partial x_j}$$

$$\underline{y} = J \Big|_Q \underline{x}$$



Jacobian


Example 8.3

$$R = 1\Omega$$

$$V_{S1} = 2V$$

$$V_{S2} = 0,2\sin(10t)$$

$$I_S = 20A$$

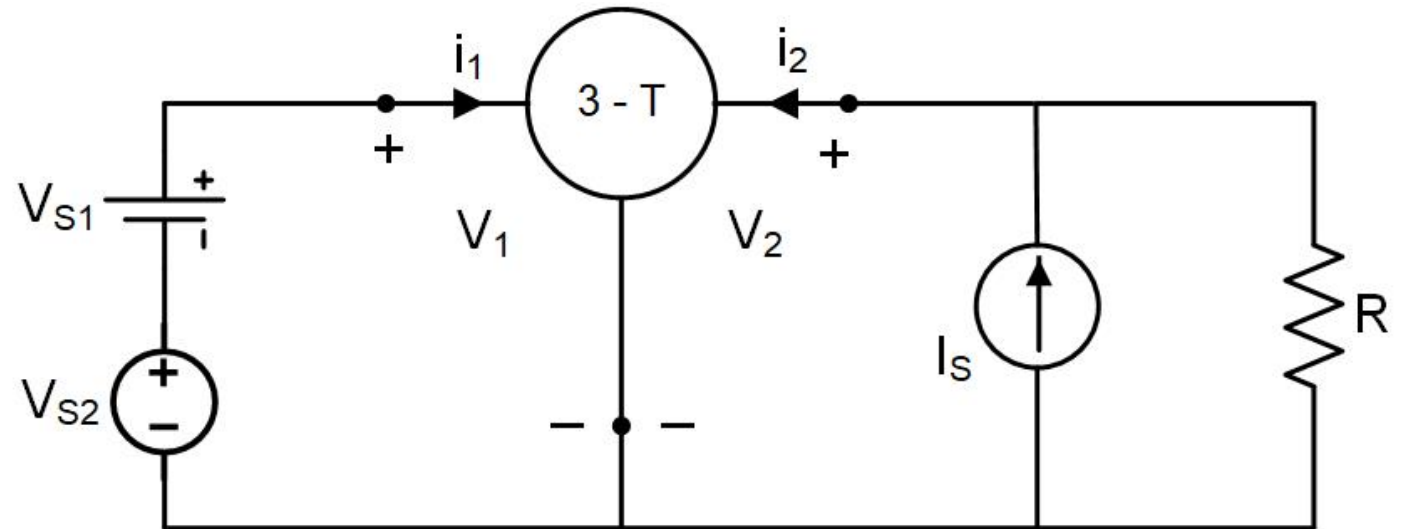


Equations of the 3 – T element:

$$V_1 = 2i_1$$
$$i_2 = v_2 + 8v_2i_1$$

Small signal components of the Ebers Moll Model of transistors


$$i_e = -I_{ES} \left(e^{-\frac{V_{eb}}{V_T}} - 1 \right) + \alpha_R I_{CS} \left(e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$
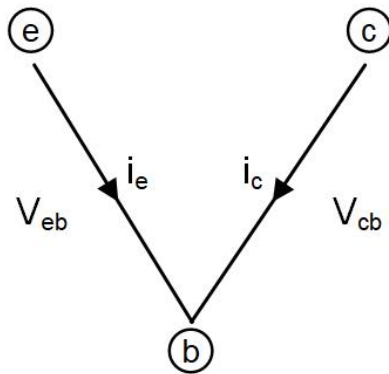
$$i_c = \alpha_F I_{ES} \left(e^{-\frac{V_{eb}}{V_T}} - 1 \right) - I_{CS} \left(e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$



$$i_e = f_1(V_{eb}, V_{cb})$$

$$i_c = f_2(V_{eb}, V_{cb})$$

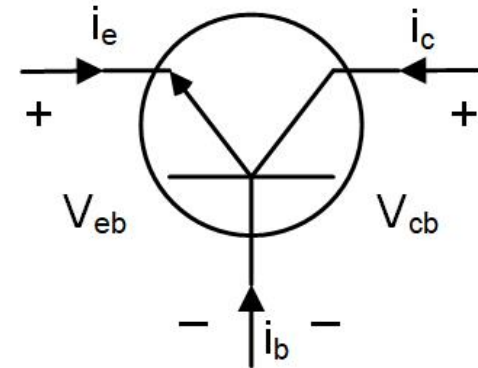

$$i_e - i_{eQ} = \left. \frac{\partial f_1}{\partial V_{eb}} \right|_Q (V_{eb} - V_{ebQ}) + \left. \frac{\partial f_1}{\partial V_{cb}} \right|_Q (V_{cb} - V_{cbQ})$$

$$i_c - i_{cQ} = \left. \frac{\partial f_2}{\partial V_{eb}} \right|_Q (V_{eb} - V_{ebQ}) + \left. \frac{\partial f_2}{\partial V_{cb}} \right|_Q (V_{cb} - V_{cbQ})$$


$$\begin{bmatrix} \widetilde{i_e} \\ \widetilde{i_c} \end{bmatrix} = \begin{bmatrix} \frac{I_{ES}}{V_T} e^{-\frac{V_{ebQ}}{V_T}} & -\frac{\alpha_R I_{CS}}{V_T} e^{-\frac{V_{cbQ}}{V_T}} \\ -\frac{\alpha_F I_{ES}}{V_T} e^{-\frac{V_{ebQ}}{V_T}} & \frac{I_{CS}}{V_T} e^{-\frac{V_{cbQ}}{V_T}} \end{bmatrix} \begin{bmatrix} \widetilde{V_{eb}} \\ \widetilde{V_{cb}} \end{bmatrix}$$

Example 8.4

$$\alpha_F = 0,99 \quad \alpha_R = 0,6$$

$$I_{CS} = 12 \text{ pA} \quad I_{ES} = 7 \text{ pA}$$
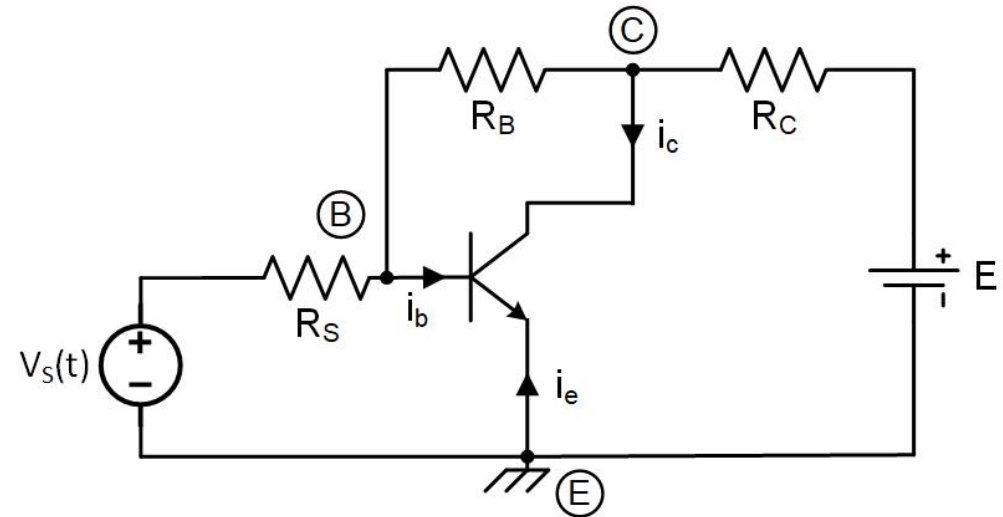
$$R_S = 600 \Omega \quad E = 15 \text{ V}$$



- Find the values of R_B and R_C such that $V_{beQ} = 0,6 \text{ V}$ and $V_{ceQ} = 5 \text{ V}$.
- Find the small signal model of the transistor around the operating point. Is the transistor locally active ?
- Find $V_{CE}(t) \cong V_{CEQ} + \tilde{V}_{CE}(t)$