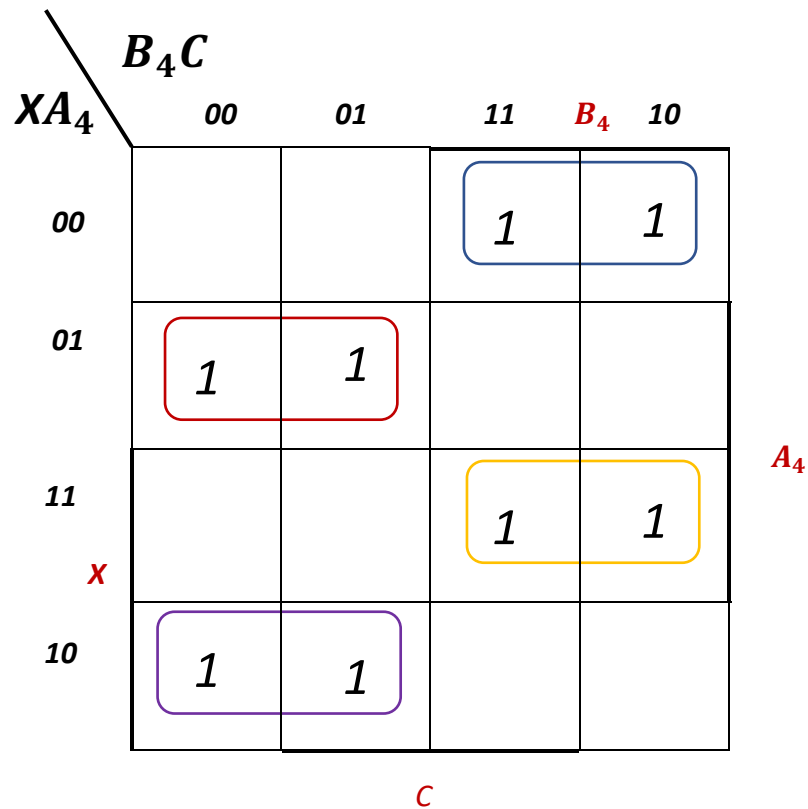


a-) Draw the truth table for the Circuit a.

X	A_4	B_4	C	O_p	R_4	Overflow
0	0	0	0	0	0	0
0	0	0	1	0	Φ	1
0	0	1	0	1	1	0
0	0	1	1	1	0	0
0	1	0	0	1	0	0
0	1	0	1	1	1	0
0	1	1	0	0	1	0
0	1	1	1	0	Φ	1
1	0	0	0	1	1	0
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	0	1	1	0	Φ	1
1	1	0	0	0	1	0
1	1	0	1	0	Φ	1
1	1	1	0	1	0	0
1	1	1	1	1	1	0

Write the simplest expression for the outputs O_p , Sign, and Overflow.


Karnaugh Map Of O_p :



Simplest Expression of O_p is $\overline{X}A_4\overline{B}_4 + \overline{X}\overline{A}_4B_4 + XA_4B_4 + X\overline{A}_4\overline{B}_4$.

TEVFIK OZGU
150180082

Karnaugh Map Of Sign :

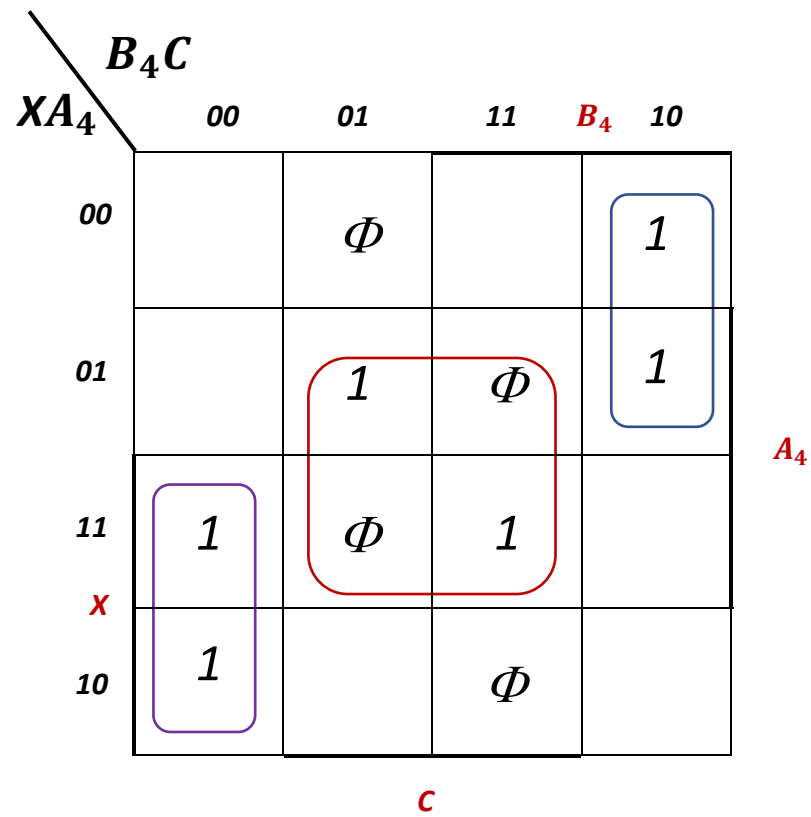

Simplest Expression of Sign is $X\bar{C}\bar{B}_4 + \bar{X}\bar{C}B_4 + CA_4$.

TEVFIK OZGU
150180082

Karnaugh Map Of Overflow :

		B_4C			
		00	01	11	10
XA_4	00		1		
	01			1	
	11		1		
	10			1	


C

A_4


Simplest Expression of Overflow is $\overline{X}\overline{A_4}\overline{B_4}C + \overline{X}A_4B_4C + XA_4\overline{B_4}C + X\overline{A_4}B_4C$.

TEVFIK OZGU
150180082

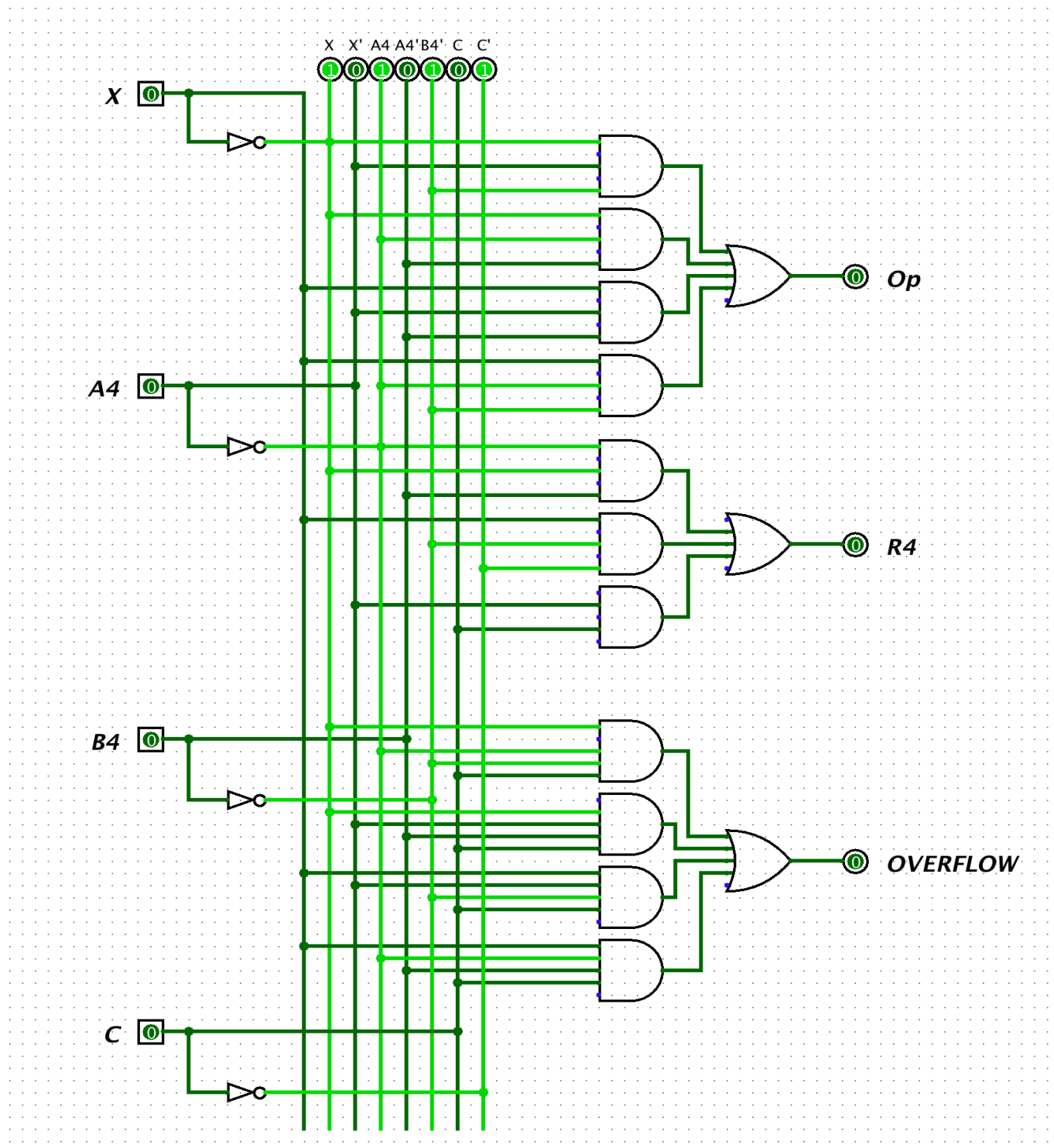Draw the circuit **a** using any type of logic gates. Fully label all input and outputs.



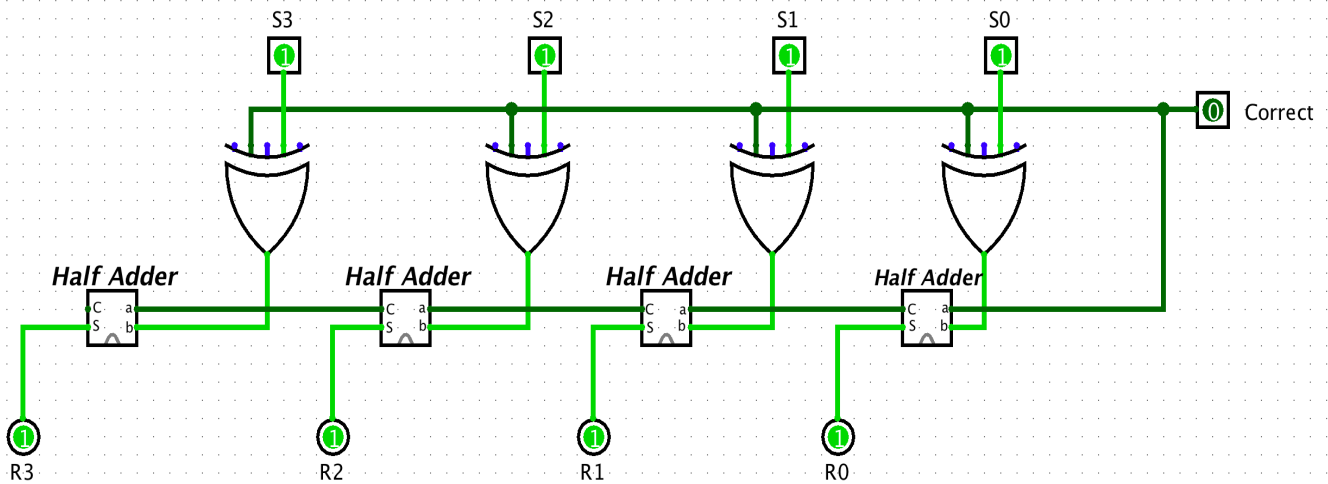b) Design and draw the Circuit c using only half adders and minimum number of logic gates. Fully label all input and outputs.



c) Design and draw the Circuit d using any type of logic gates. Fully label all input and outputs.

