

Node Analysis

Assumption: the elements are v-controlled

1. Write current (branch) equations at nodes (KCL)
2. Write element (branch) currents in terms of element (branch) voltages
3. Replace element (branch) voltages with node-to-datum voltages

$$\textcircled{1} \quad i_1 + i_5 - I_{S1} = 0$$

$$\textcircled{2} \quad -i_1 + i_2 + i_3 + I_{S2} = 0$$

$$\textcircled{3} \quad -i_2 + i_4 - i_5 = 0$$

$$\textcircled{1} \quad G_1 V_1 + \dots = 0$$


$$\textcircled{2} \quad -G_1 V_1 + \dots = 0$$

$$\textcircled{3} \quad -G_2 V_2 + \dots = 0$$

$$\textcircled{1} \quad G_1(e_1 - e_2) + \dots = 0$$

$$\textcircled{2} \quad -G_1(e_1 - e_2) + \dots = 0$$
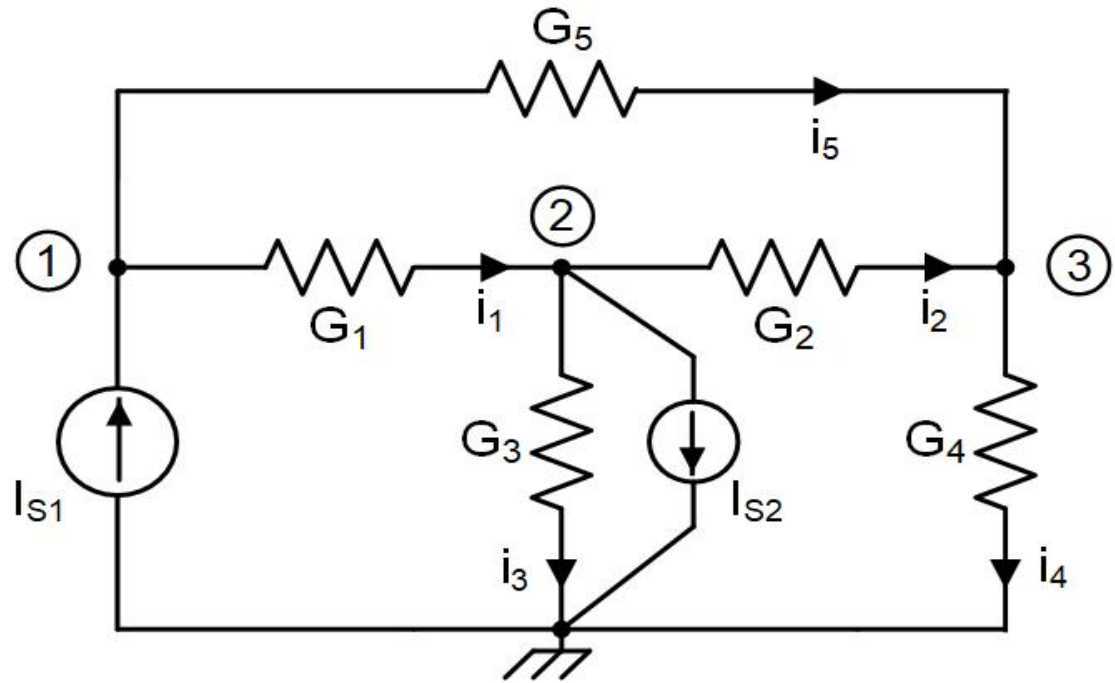
$$\textcircled{3} \quad -G_2(e_2 - e_3) + \dots = 0$$



$$\underbrace{\begin{bmatrix} G_1 + G_5 & -G_1 & -G_5 \\ -G_1 & G_1 + G_2 + G_3 & -G_2 \\ -G_5 & -G_2 & G_2 + G_4 + G_5 \end{bmatrix}}_{\mathbf{Y}_n} \underbrace{\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}}_{\mathbf{e}} = \underbrace{\begin{bmatrix} I_{S1} \\ -I_{S2} \\ 0 \end{bmatrix}}_{\mathbf{I}_S}$$

\mathbf{Y}_n : node admittance matrix

\mathbf{I}_S : equivalent source vector

Properties:

1. The k th diagonal element of \mathbf{Y}_n is equal to the sum of all conductances attached to node k .
2. The k th off-diagonal element of \mathbf{Y}_n is equal to the negative of the sum of the conductances between node j and node k .
3. The k th element of \mathbf{I}_S is equal to the algebraic sum of currents of all independent current sources entering node k .
4. The matrix \mathbf{Y}_n is symmetric ($\mathbf{Y}_n = \mathbf{Y}_n^T$).

Modified node analysis


If there are also elements which are not v-controlled.

1. Write node equations using node voltages as variables.
2. Whenever an element is encountered that is not v-controlled, introduce in the node equation the corresponding branch current as a new variable.
3. Add the branch equation of that element as a new equation. The voltages of the elements which are not v-controlled, are written in terms of node voltages.

$$\textcircled{1} \quad i_1 + i_5 + i_7 = 0$$

$$\textcircled{2} \quad -i_1 + i_2 + i_3 + I_{S2} = 0$$
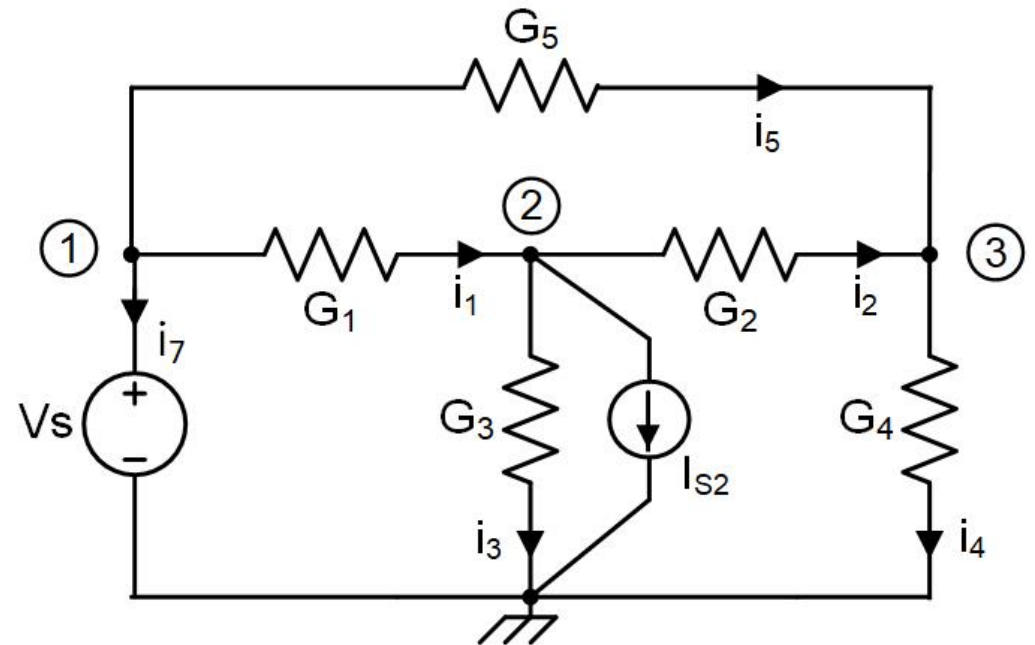
$$\textcircled{3} \quad -i_2 + i_4 - i_5 = 0$$



$$\textcircled{1} \quad G_1(e_1 - e_2) + G_5(e_1 - e_3) + i_7 = 0$$


$$\textcircled{2} \quad -G_1(e_1 - e_2) + G_2(e_2 - e_3) + G_3e_2 = -I_{S2}$$

$$\textcircled{3} \quad -G_2(e_2 - e_3) - G_5(e_1 - e_3) + G_4e_3 = 0$$

Extra equation: $e_1 = V_S$

$$\begin{bmatrix} G_1 + G_5 & -G_1 & -G_5 & 1 \\ -G_1 & G_1 + G_2 + G_3 & -G_2 & 0 \\ -G_5 & -G_2 & G_1 + G_4 + G_5 & 0 \\ 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ i_7 \end{bmatrix} = \begin{bmatrix} 0 \\ -I_{S2} \\ 0 \\ V_S \end{bmatrix}$$

Example 4.1

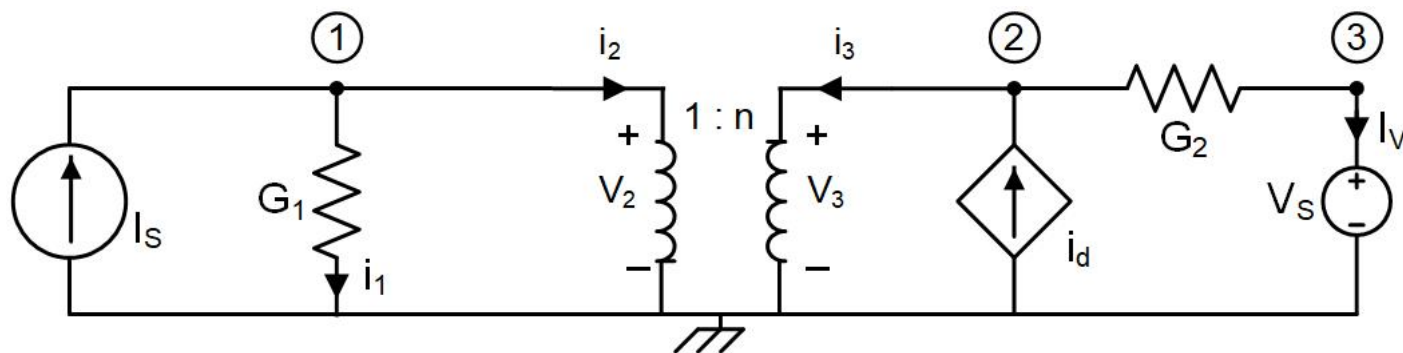

$$i_d = \alpha i_1$$

$$\begin{bmatrix} G_1 & 0 & 0 & 1 & 0 & 0 \\ -\alpha G_1 & G_2 & -G_2 & 0 & 1 & 0 \\ 0 & -G_2 & G_2 & 0 & 0 & 1 \\ -n & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & n & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ i_2 \\ i_3 \\ I_V \end{bmatrix} = \begin{bmatrix} I_S \\ 0 \\ 0 \\ 0 \\ 0 \\ V_S \end{bmatrix}$$