

## Circuit Elements

$$\phi(t) = \phi(t_0) + \int_{t_0}^t v(\tau) d\tau \quad v(t) = \frac{d\phi(t)}{dt}$$

$$q(t) = q(t_0) + \int_{t_0}^t i(\tau) d\tau \quad i(t) = \frac{dq(t)}{dt}$$

$f(v,i,t) = 0 \rightarrow$  resistor

$f(\phi,i,t) = 0 \rightarrow$  inductor

$f(v,q,t) = 0 \rightarrow$  capacitor

$f(q,\phi,t) = 0 \rightarrow$  memristor

The equations describing the characteristics are called *element equations* or *branch equations*.

$f(x,y,t)$  : characteristic of the element       $x,y \in \{i, v, q, \phi\}$        $x,y$ : proper pair

$y = h(x,t)$  :       $x$ -controlled

$x = g(y,t)$  :       $y$ -controlled

Time – invariance: For each  $(x,y)$  and  $t_0$ ,  $[x(t - t_0), y(t - t_0)]$  is a proper pair.

Linearity: If for each  $(x_1, y_1)$  and  $(x_2, y_2)$  proper pairs and for each  $\mu \in \mathbb{R}$

1)  $(x_1 + x_2, y_1 + y_2)$  is also a proper pair and

2)  $(\mu x_1, \mu y_1)$  is also a proper pair,

Then the circuit element is linear; otherwise nonlinear.

Bilateral property: For each proper pair  $(x, y)$ ,  $(-x, -y)$  is also a proper pair.

For a bilateral resistor:  $f(v, i) = f(-v, -i)$

Example 2.1: Diode  $i = I_s \left( e^{v/V_T} - 1 \right)$   $I_s = (\text{nA}, \mu\text{A})$   $V_T = 26\text{mV}$

## Two – terminal resistor

$$v(t) = f(i(t)) \text{ or } i(t) = g(v(t))$$

*Linear resistor:*  $v = Ri$  or  $i = Gv$   $R$ : resistance  $[\Omega]$

$G$ : conductance  $[\text{U}, mho, S]$



*Nonlinear resistor:*  $v(t) = f(i(t))$

$$v(t) = v_0 + \left. \frac{df}{di} \right|_{I_0} (i(t) - I_0)^2 + \dots$$

$R_d$ : differential resistor



## Two – terminal inductor

$$\phi(t) = f(i(t)) \text{ or } i(t) = g(\phi(t))$$

$$\text{Linear inductor: } \phi(t) = Li(t) \rightarrow v(t) = L \frac{di(t)}{dt}$$


L: inductance [H]



$$\text{Nonlinear inductor: } \phi(t) = \phi(0) + \int_0^t v(\tau) d\tau$$



Hysteresis:

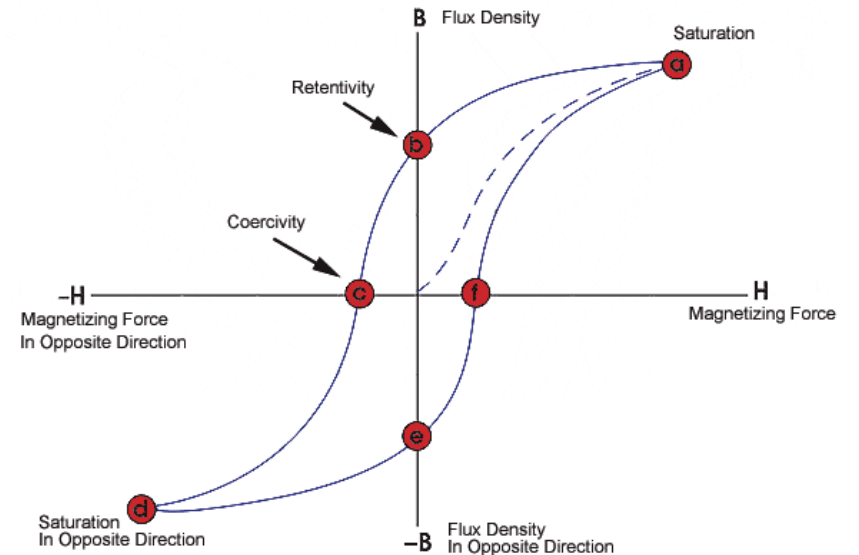


## Two – terminal capacitor

$$q(t) = f(v(t)) \text{ or } v(t) = g(q(t))$$


Linear capacitor:  $q(t) = Cv(t) \rightarrow C$ : capacitance [F]

$$\frac{dq(t)}{dt} = i(t) = C \frac{dv(t)}{dt}$$

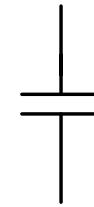$v(t) = Sq(t) \rightarrow S$ : elastance [ $F^{-1}$ ]



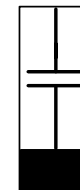Nonlinear capacitor:  $q(t) = q(0) + \int_0^t i(\tau) d\tau$



## Open circuit and short circuit

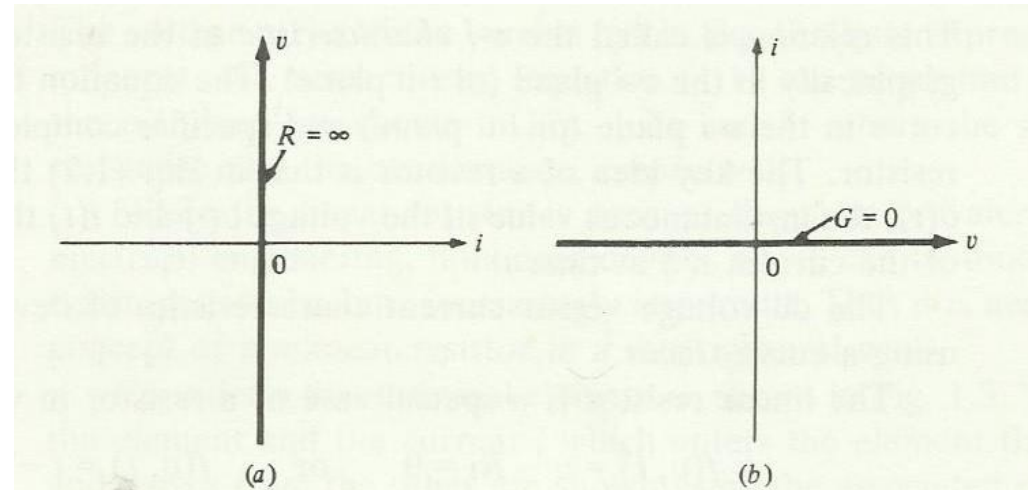


Figure 1.4 Characteristic of an open circuit.

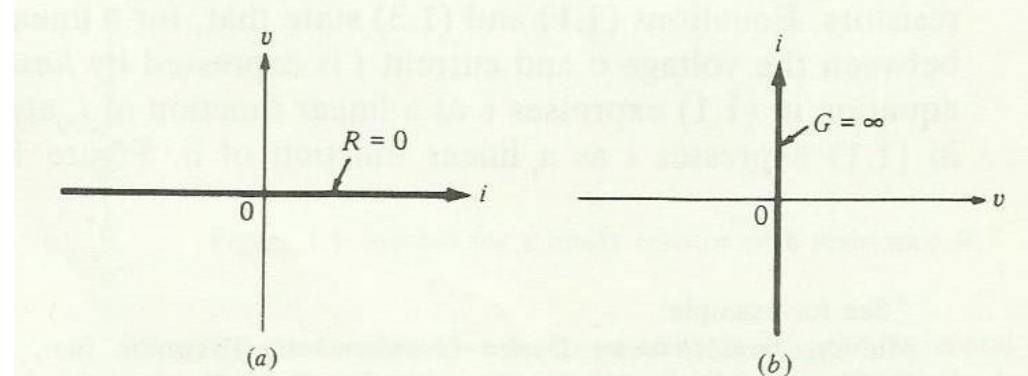



Figure 1.5 Characteristic of a short circuit.

open circuit:  $i = 0$

short circuit:  $v = 0$

The *dual* of a given resistor is another resistor whose  $v - i$  characteristics in the  $v - i$  plane is the same curve as that of the given resistor in the  $i - v$  plane.



Nullator:  $v = 0$   $i = 0$

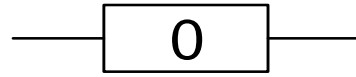

Norator:  $0v + 0i = 0$




$v = \dots$   $i = \dots$

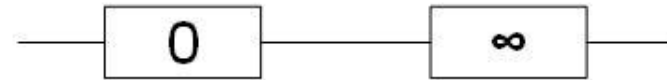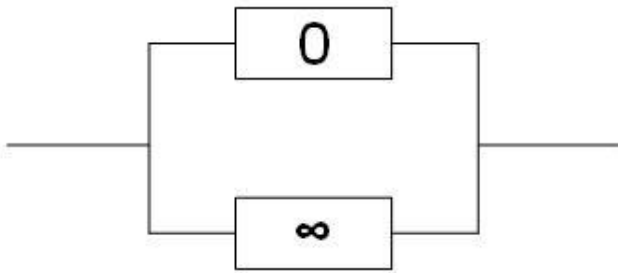


**Independent Sources** are circuit elements which can supply a specified voltage or current that is independent of a current or voltage elsewhere in the circuit.

*Independent voltage source*
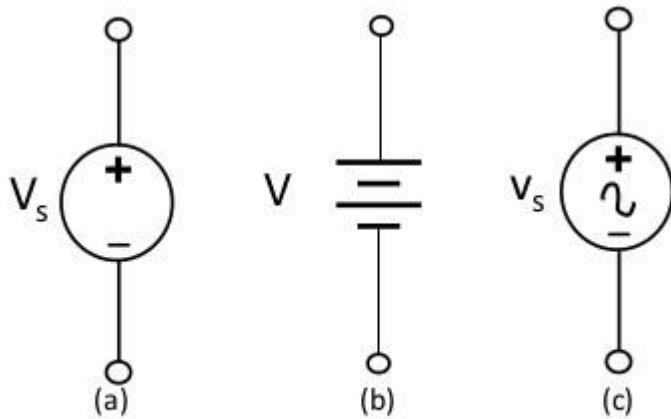
$$\mathcal{R}_{v_s} = \{(v, i): v = v_s(t) \text{ for } -\infty < i < \infty\}$$




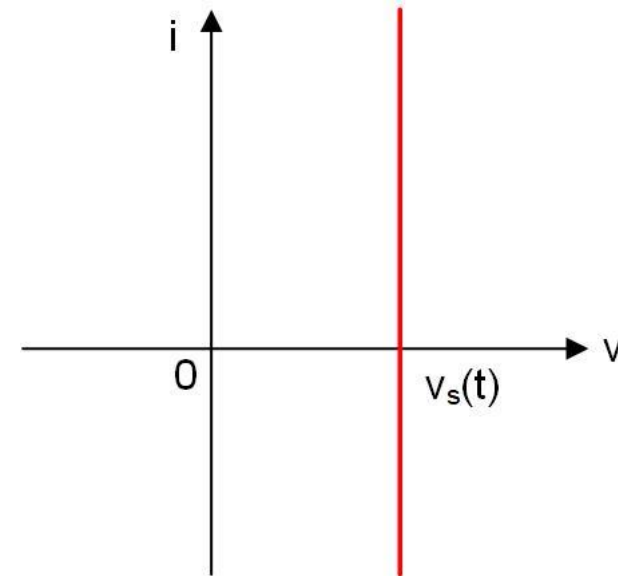
(a) and (b) DC independent voltage source symbols. (c) AC independent voltage source symbol.






*Independent current source*

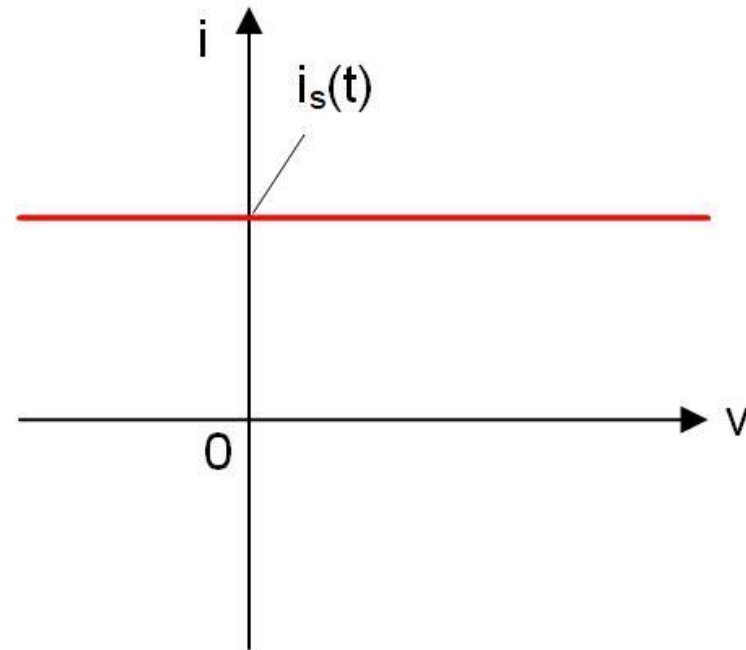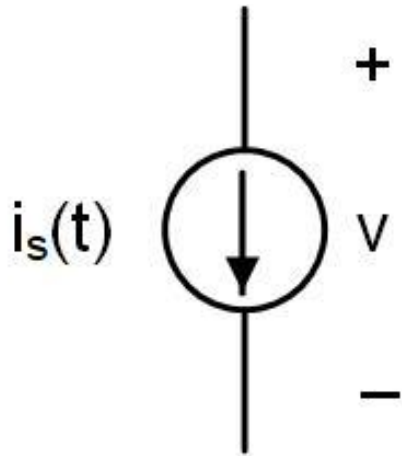
$$\mathcal{R}_{i_s} = \{(v, i): i = i_s(t) \text{ for } -\infty < v < \infty\}$$



## Series connection of resistors

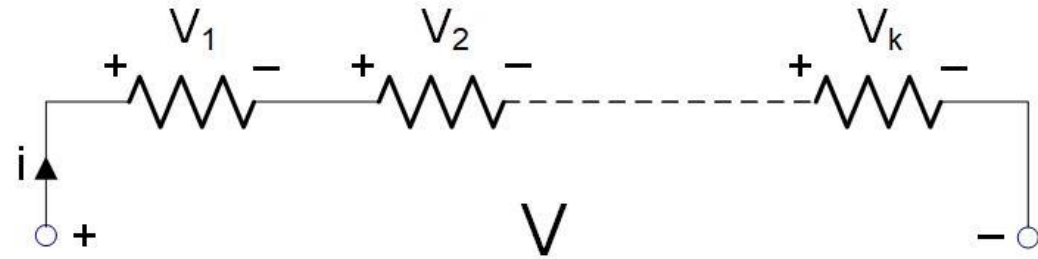


## Parallel connection of resistors

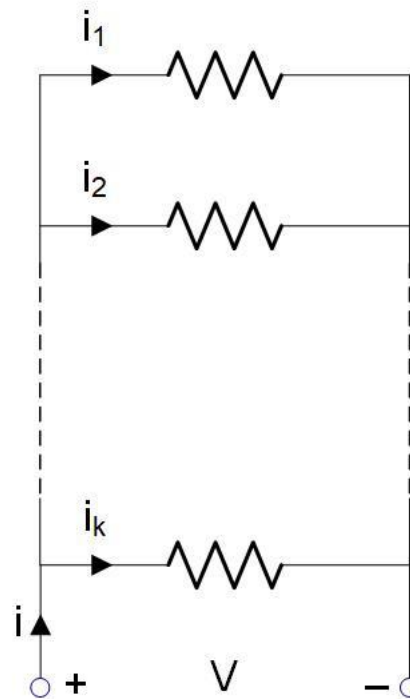


Independent voltage sources in series


$$v = \sum_{j=1}^m v_j$$

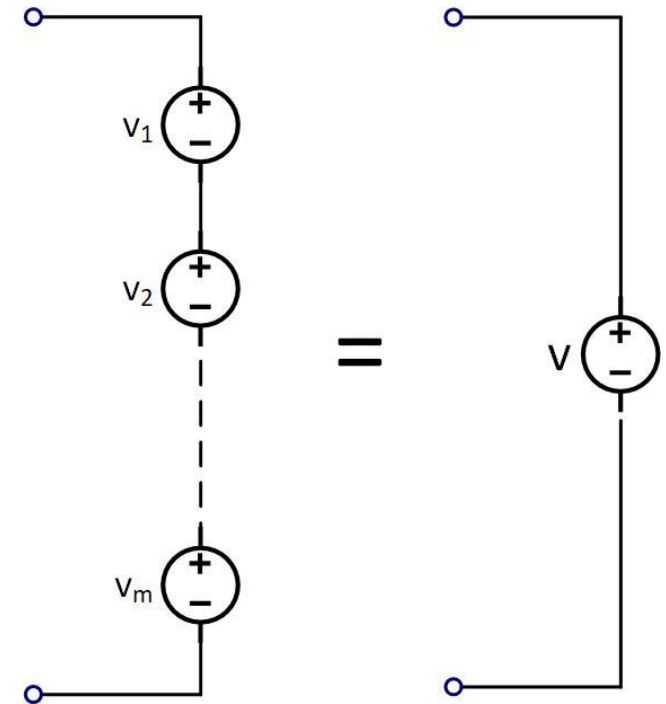

Parallel connection of independent current sources



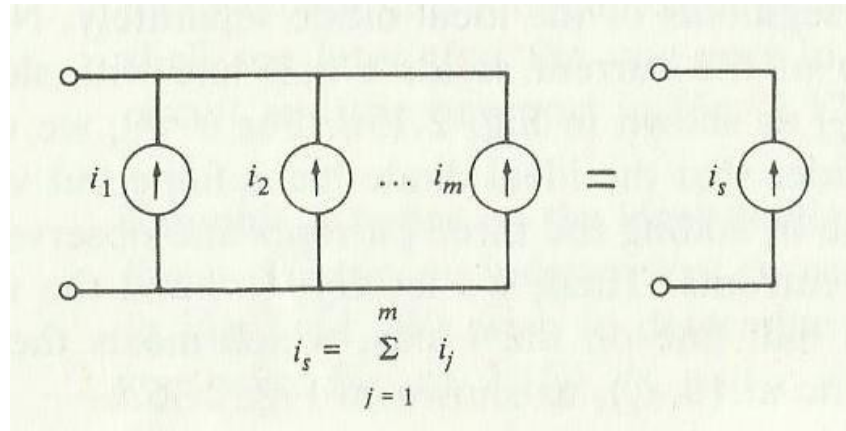


Example 2.2:

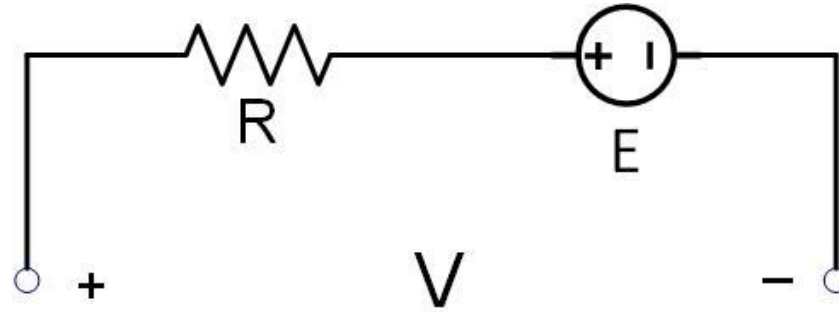


*The Diode*  $i = I_s \left( e^{v/v_T} - 1 \right)$



$I_s = (\text{nA}, \mu\text{A}) \quad V_T = 26\text{mV}$

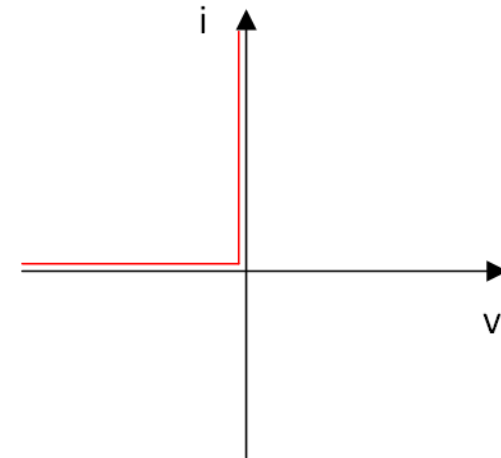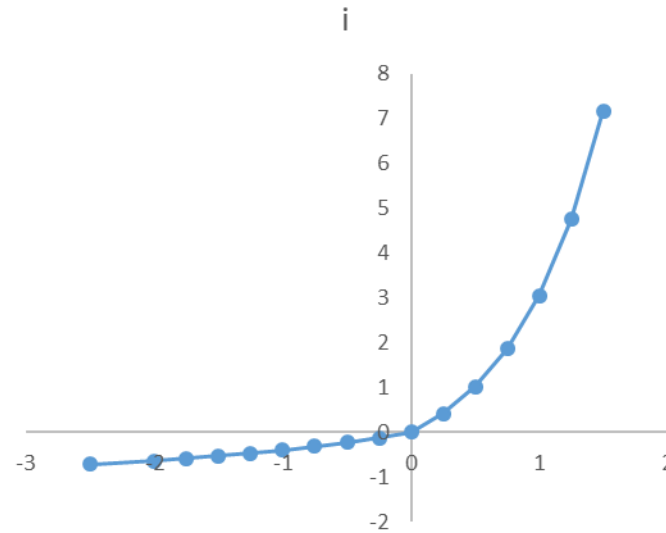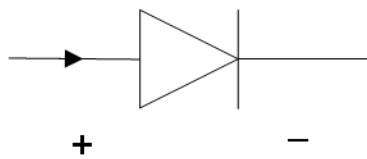


Example 2.3:

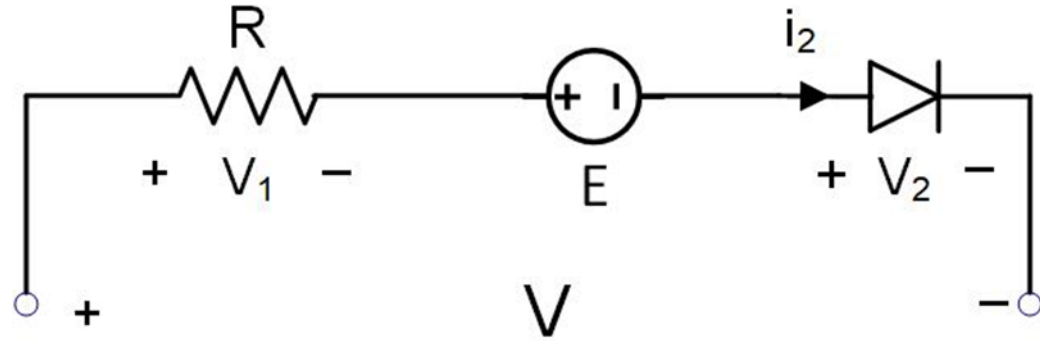

*Zener diode*

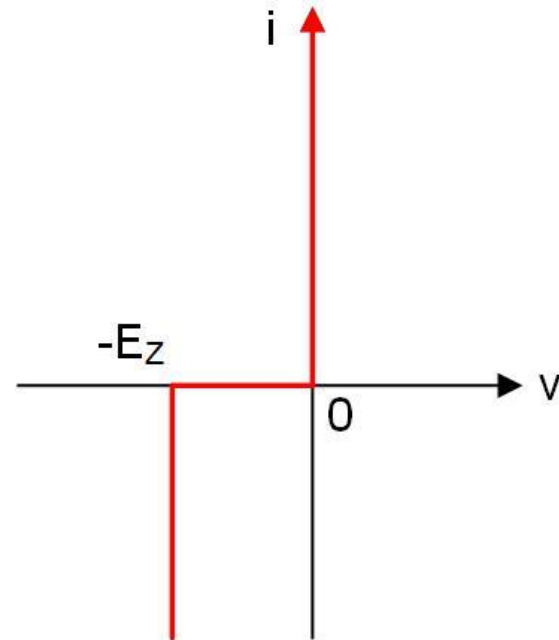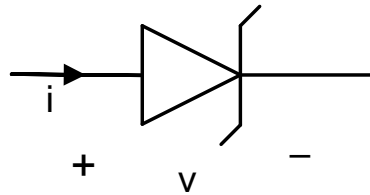



## *The tunnel diode*

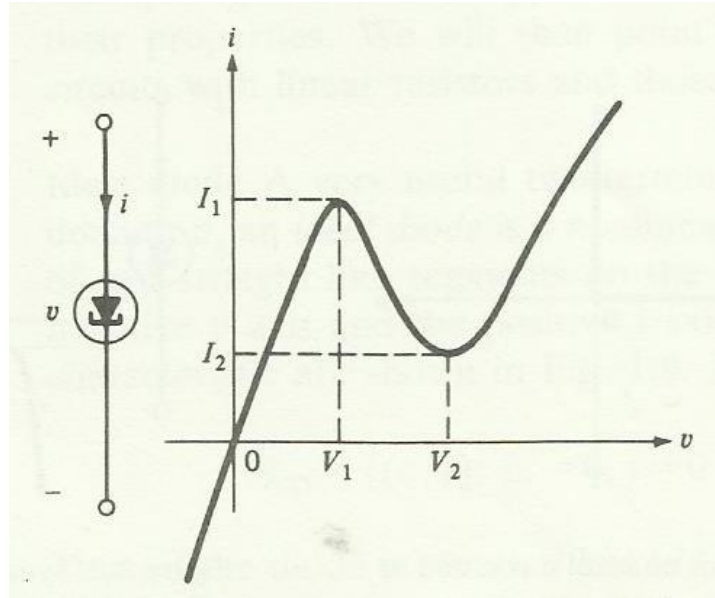

$i$  – controlled or  $v$  – controlled ?



*Reverse bias*

Symmetric w.r.t.  
origin.

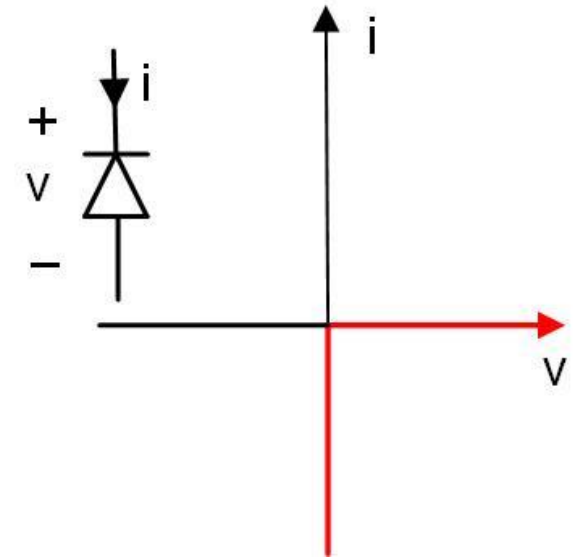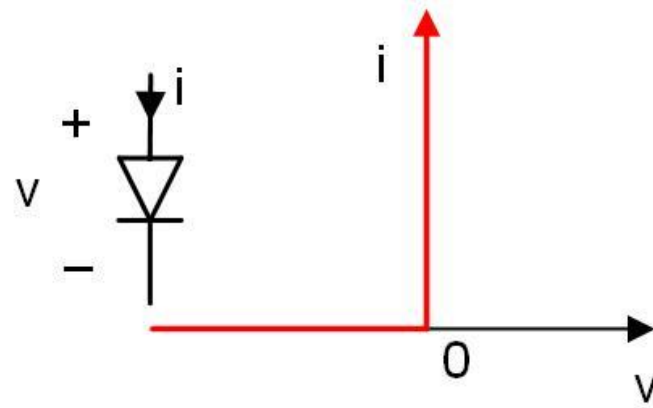


*Axis exchange*

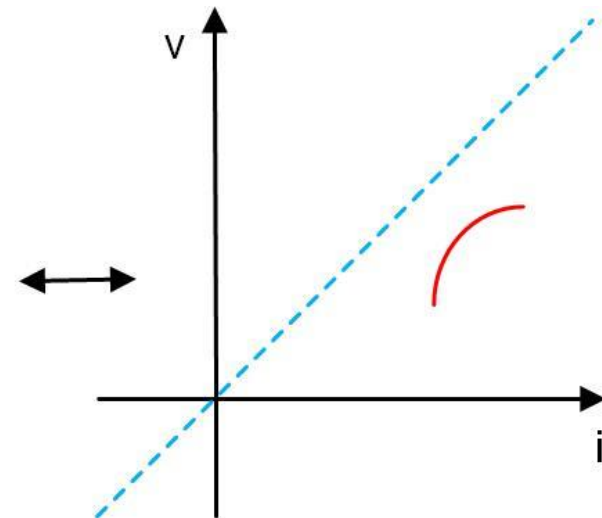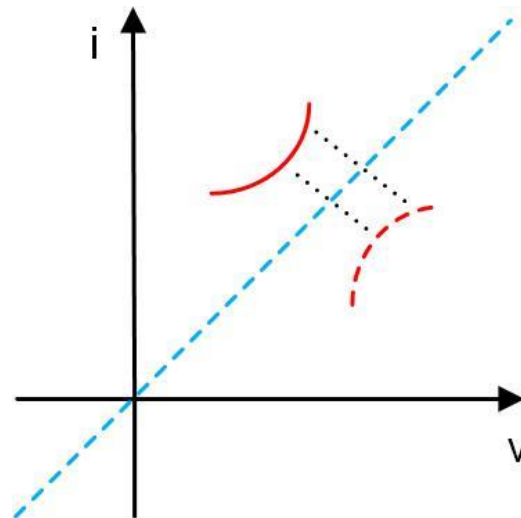Symmetric w.r.t. the line  
with  $45^\circ$  slope.



## Resistive Two-Ports

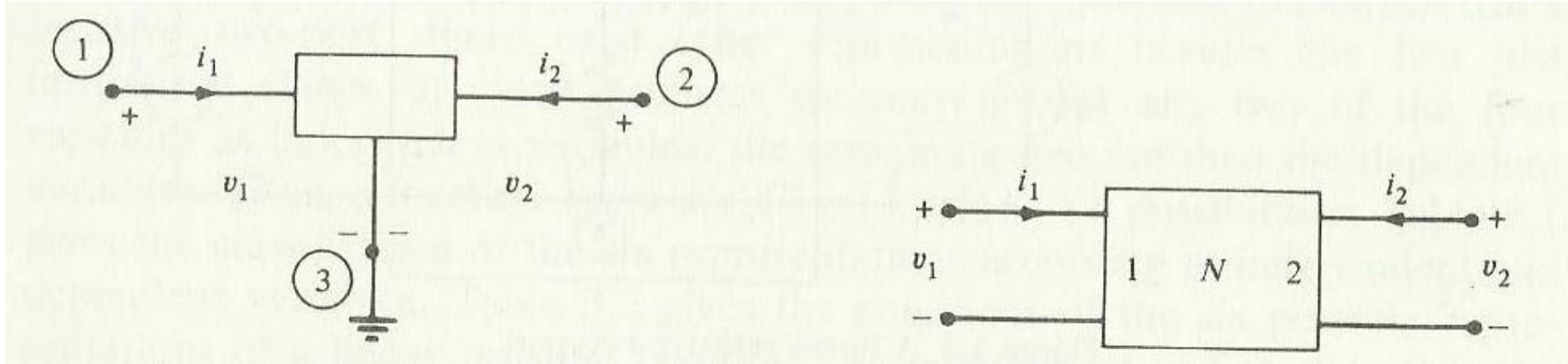


A three-terminal element or a two-port will be called a resistor if its port voltages and currents satisfy the following relation:

$$\mathcal{R}_R = \{(v_1, v_2, i_1, i_2) : f_1(v_1, v_2, i_1, i_2) = 0 \text{ and } f_2(v_1, v_2, i_1, i_2) = 0\}$$



## Example 2.4

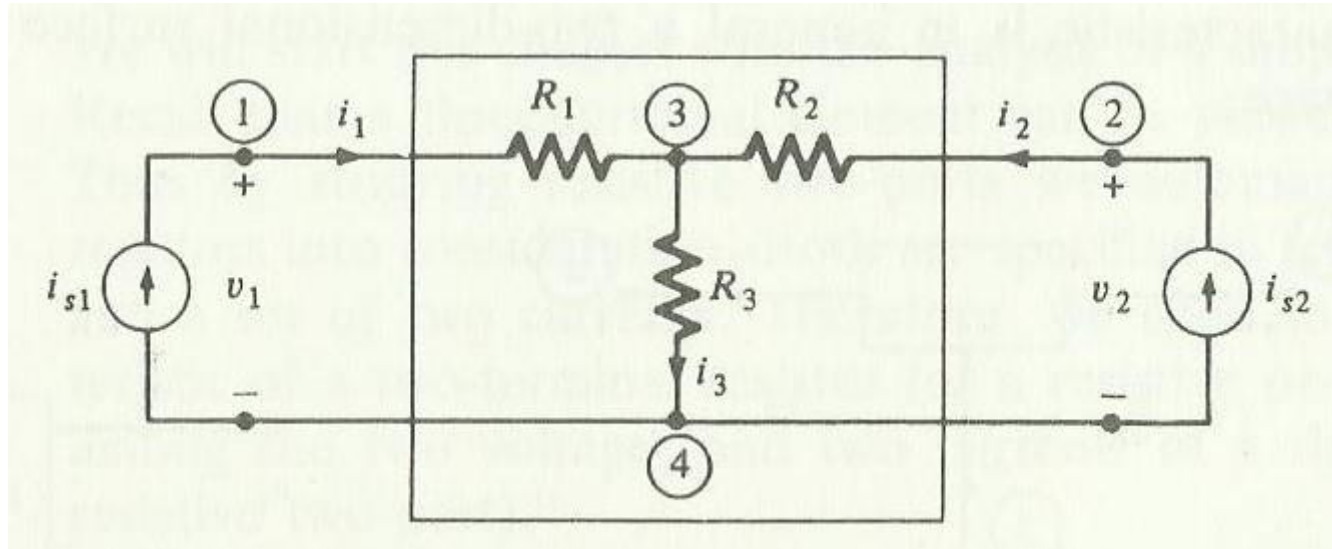

$$\mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \mathbf{R}\mathbf{i} = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

## Equations for the six representations of a linear resistive two-port

Representations	Scalar equations	Vector equations
Current-controlled	$v_1 = r_{11}i_1 + r_{12}i_2$ $v_2 = r_{21}i_1 + r_{22}i_2$	$\mathbf{v} = \mathbf{R}\mathbf{i}$
Voltage-controlled	$i_1 = g_{11}v_1 + g_{12}v_2$ $i_2 = g_{21}v_1 + g_{22}v_2$	$\mathbf{i} = \mathbf{G}\mathbf{v}$
Hybrid 1	$v_1 = h_{11}i_1 + h_{12}v_2$ $i_2 = h_{21}i_1 + h_{22}v_2$	$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = H \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$
Hybrid 2	$i_1 = h'_{11}v_1 + h'_{12}i_2$ $v_2 = h'_{21}v_1 + h'_{22}i_2$	$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = H' \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$
Transmission 1	$v_1 = t_{11}v_2 - t_{12}i_2$ $i_1 = t_{21}v_2 - t_{22}i_2$	$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = T \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$
Transmission 2	$v_2 = t'_{11}v_1 + t'_{12}i_1$ $-i_2 = t'_{21}v_1 + t'_{22}i_1$	$\begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} = T' \begin{bmatrix} v_1 \\ i_1 \end{bmatrix}$

# Resistive two-ports

## Linear Controlled Sources

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ r_m & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$r_m$ : transresistance

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$g_m$ : transconductance

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \alpha & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

$\alpha$ : current transfer ratio


$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \mu & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$\mu$ : voltage transfer ratio

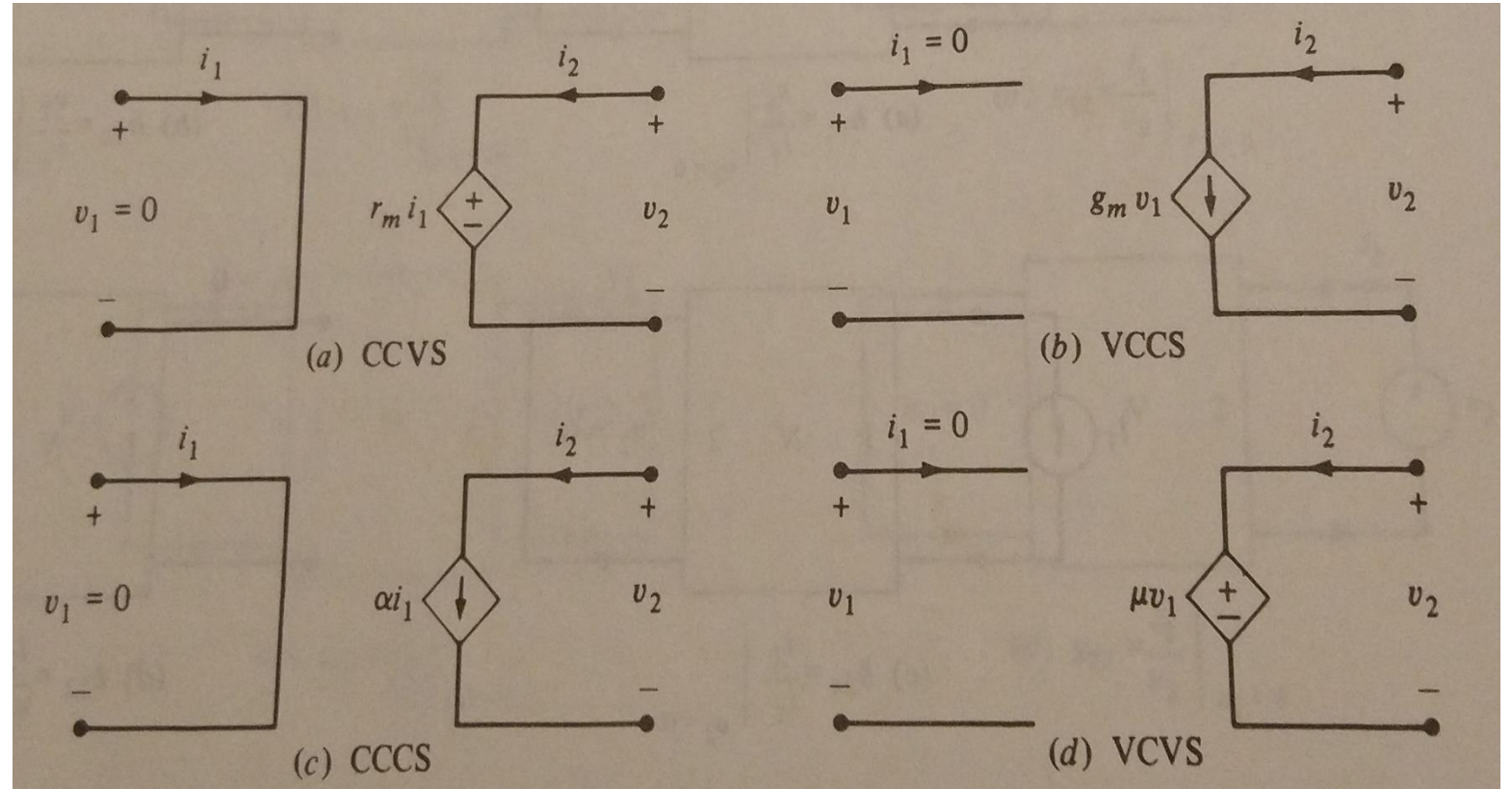

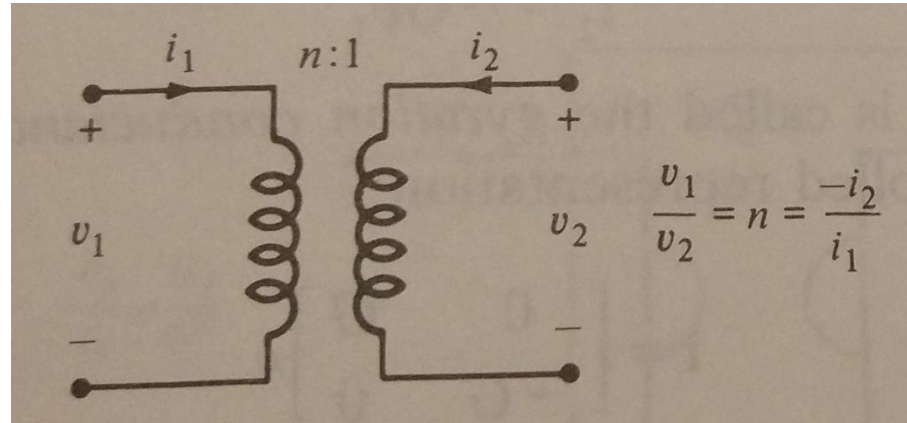
## Ideal transformer

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & n \\ -n & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$


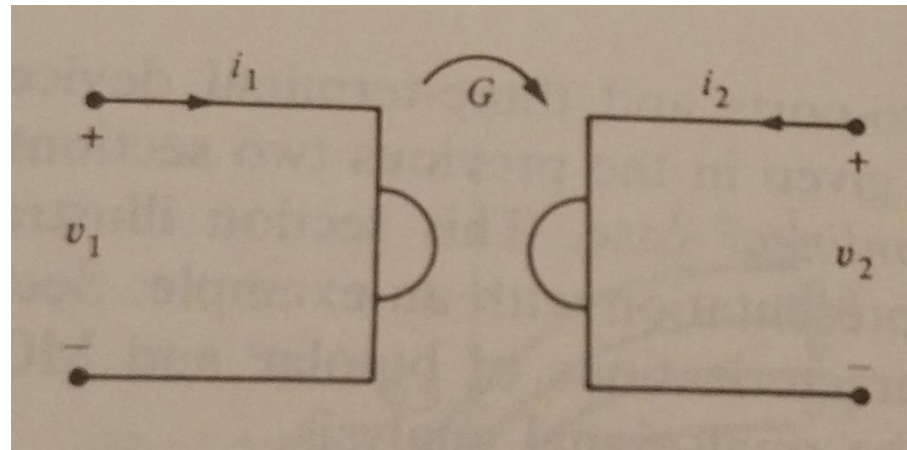
## Gyrator

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & G \\ -G & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$




## Mutual Inductor

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$L_1, L_2$  : self inductance

$M$ : mutual inductance

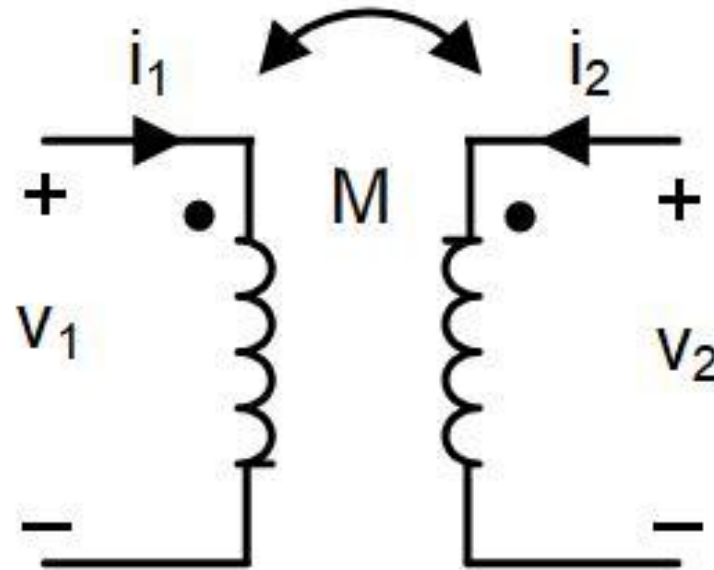

## The npn Bipolar Transistor

$$i_e = -I_{ES} \left( e^{-\frac{V_{eb}}{V_T}} - 1 \right) + \alpha_R I_{CS} \left( e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$

$$i_c = \alpha_F I_{ES} \left( e^{-\frac{V_{eb}}{V_T}} - 1 \right) - I_{CS} \left( e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$

$$\alpha_R = 0,5 \dots 0,8$$


$$I_{ES}, I_{CS} = 10^{-12} \dots 10^{-10} \text{ at } 25^\circ\text{C}$$

$$V_T \approx 26 \text{ mV at } 25^\circ\text{C}$$

$$i_1 = I_{ES} \left( e^{-\frac{V_{eb}}{V_T}} - 1 \right)$$

$$i_2 = I_{CS} \left( e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$
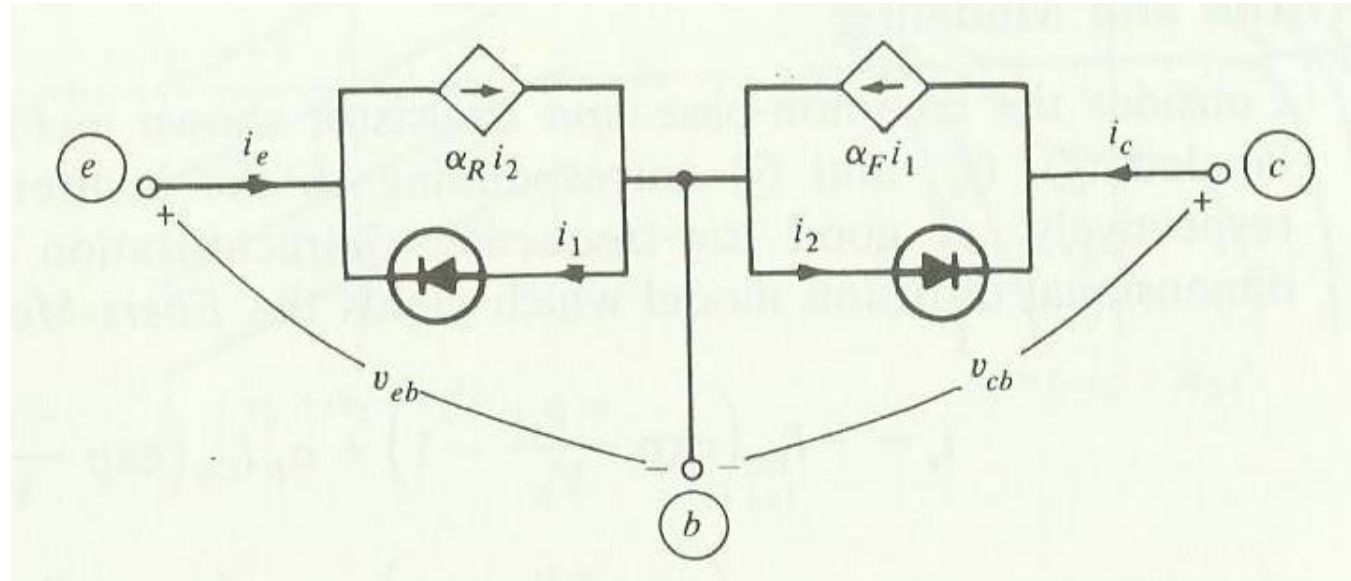
## Ebers Moll circuit model of npn transistor



$$i_1 = I_{ES} \left( e^{-\frac{V_{eb}}{V_T}} - 1 \right)$$



$$i_2 = I_{CS} \left( e^{-\frac{V_{cb}}{V_T}} - 1 \right)$$

$$i_e + i_1 = \alpha_R i_2$$

$$i_c + i_2 = \alpha_F i_1$$

# Operational amplifier (Opamp)

## Ideal opamp model

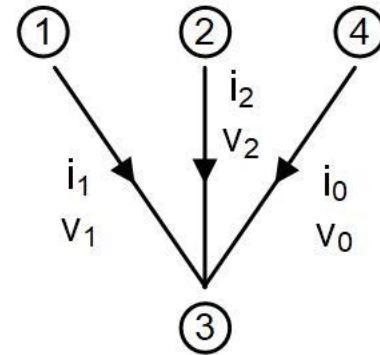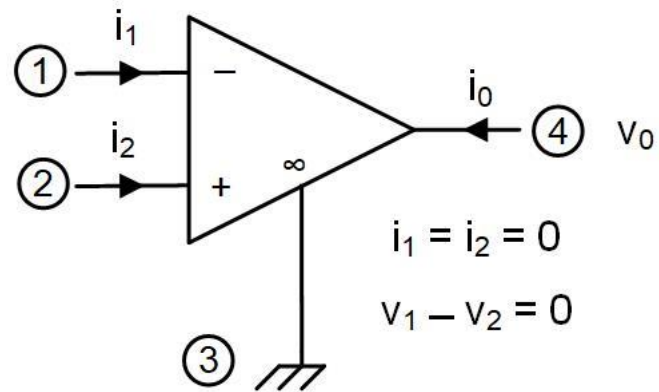





# Source Function Types
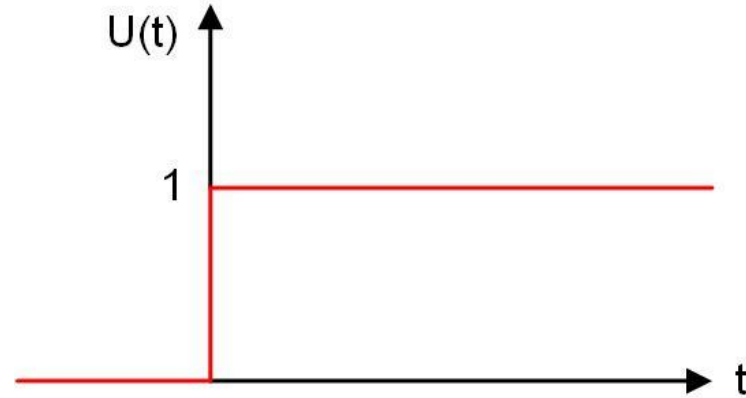
## Unit step function

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$



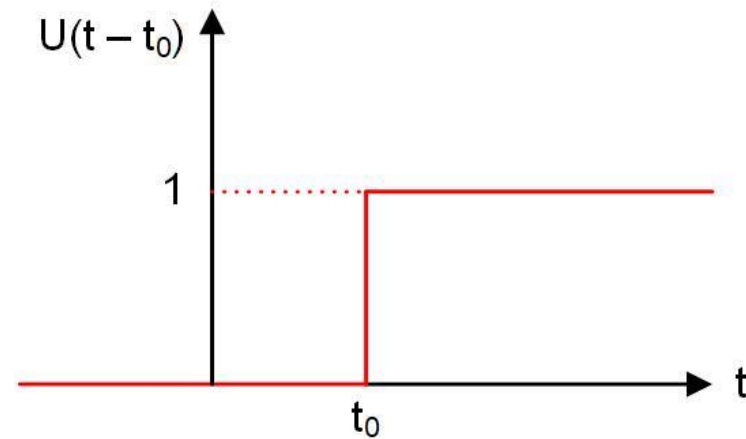
$$u(t - t_0) = \begin{cases} 1 & t \geq t_0 \\ 0 & t < t_0 \end{cases}$$



## Pulse function

$$p(t) = \begin{cases} 1 & 0 \leq t < t_0 \\ 0 & t < 0, t \geq t_0 \end{cases}$$


$$p(t) = u(t) \dots$$

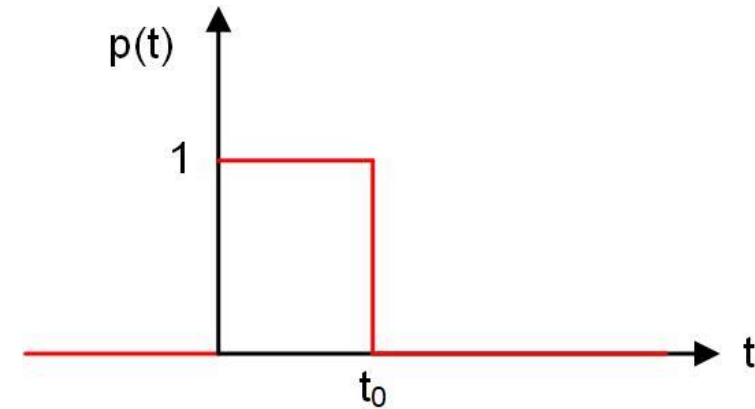
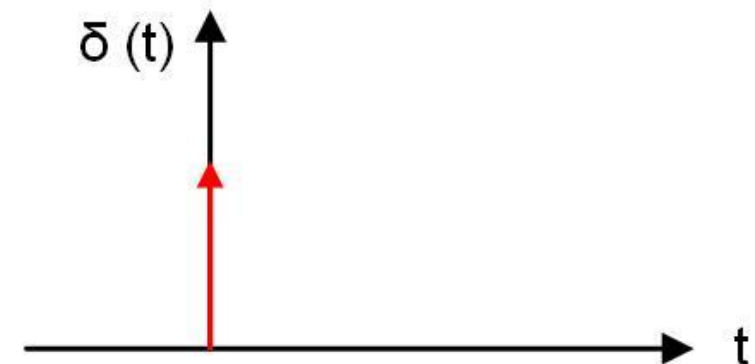
## Unit impuls function

$$\delta(t) \triangleq \begin{cases} \text{singular} & t = 0 \\ 0 & t \neq 0 \end{cases}$$

$$\int_{\varepsilon_2}^{\varepsilon_1} \delta(t) dt = 1 \quad \text{for any } \varepsilon_1 > 0 \text{ and } \varepsilon_2 < 0$$



## Periodic functions

$$x(t) = x(t+T)$$

T: period [s]


f:  $1/T$  [Hz,  $s^{-1}$ ]

$$x(t) = X_m \cos(\omega t + \varphi)$$

$X_m$ : amplitude

$\omega$ : angular frequency

$\varphi$ : phase angle

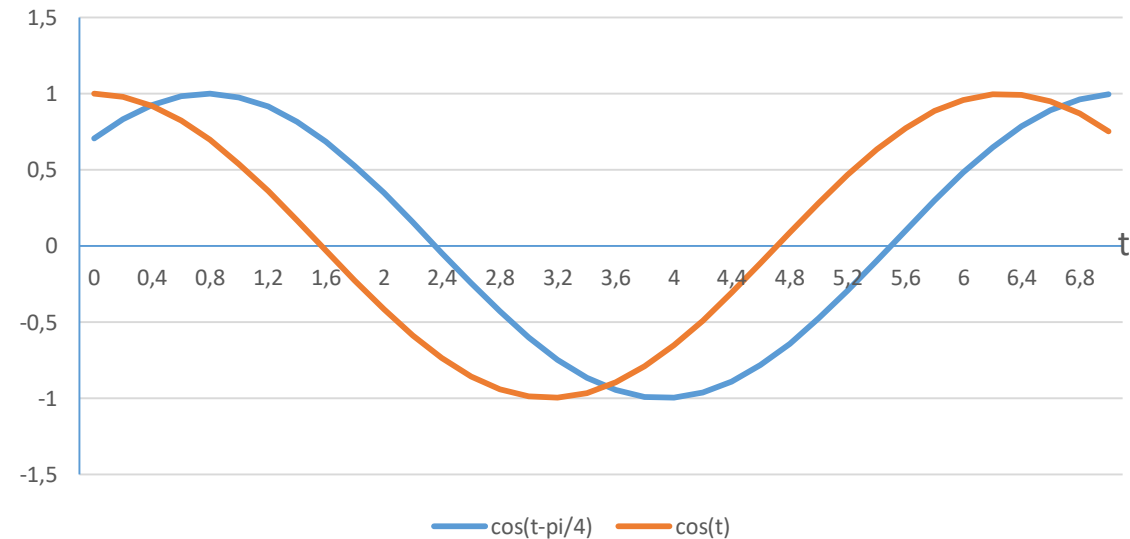

Mean value:  $\bar{x} = \frac{1}{T} \int_{t_0}^{t_0+T} x(t) dt$

Effective value:  $x_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x(t)^2 dt}$

Example 2.5  $x(t) = \begin{cases} 3 & 0 \leq t \leq 2 \\ -1 & 2 < t \leq 3 \end{cases}$   $x(t) = x(t+3)$

## Energy, Active and Passive Elements

Energy delivered to the element in the interval  $(t_0, t)$

$$E(t_0, t) = \int_{t_0}^t \mathbf{v}(t)^T \mathbf{i}(t) dt$$

Energy delivered from the element to the remainder of the circuit in the interval  $(t_0, t)$

$$E(t_0, t) = - \int_{t_0}^t \mathbf{v}(t)^T \mathbf{i}(t) dt$$

$$E(t) = E(t_0) + \int_{t_0}^t \mathbf{v}(t)^T \mathbf{i}(t) dt$$

If  $E(t) = \int_{t_0}^t \mathbf{v}(t)^T \mathbf{i}(t) dt \geq 0$  the element is **passive**.

If  $E(t)$  is an increasing function for a passive element  $\rightarrow$  energy is delivered to this element all the time

If the function becomes negative for some  $t$  values  $\rightarrow$  the element is **active**

Example 2.6 linear resistor,  $R > 0$

$$P = \mathbf{v} \mathbf{i} = (R \mathbf{i}) \mathbf{i} = R \mathbf{i}^2 \qquad E(t) = \int_{t_0}^t i^2 R dt > 0 \rightarrow \text{passive}$$