

Rules:


- 1) Your homework should be hand-written.
- 2) Don't include a cover page. Use both sides of the paper.
- 3) Have at least 1,5 cm margin from the edges.
- 4) The grades of identical or very similar looking homeworks will be divided to the number of such homeworks.
- 5) Your homeworks will be collected in the class on Wednesdays before the first lecture, till 12:30. If you bring your homework between 12:31 – 13:30 your grade will be multiplied with 0,7. After 13:30 no homework will be accepted.
- 6) You must sign on a sheet of paper as proof of handing in.

If you want to hand in your homework before Wednesday, you must contact research assistant Görkem Yazgaç (Office: 8301).

1-a) Find the operating point of the nonlinear resistor. Take the positive root as the solution of the second degree equation. (Hint: First you may find Thevenin equivalent of the linear part of the circuit.) (100 points)

1-b) Find small signal components of the nonlinear resistor and write approximate $V_R(t)$ and $i_R(t)$. (40 points)

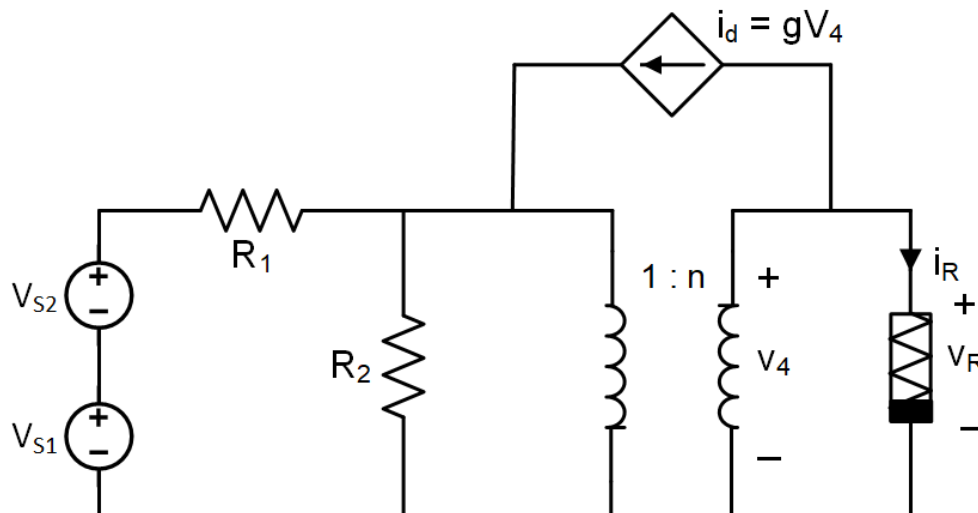
$$(R_1 = 1\Omega, R_2 = 1\Omega, V_{S1} = 4V, V_{S2} = 0,2\sin(5t) V, n = 2, g = 3S, V_R = i_R^2 - \frac{7}{2}i_R - 3)$$



2-a) Find the operating point of the nonlinear 3-T element. (30 points)

2-b) Find small signal components of the nonlinear 3-T element. (60 points)
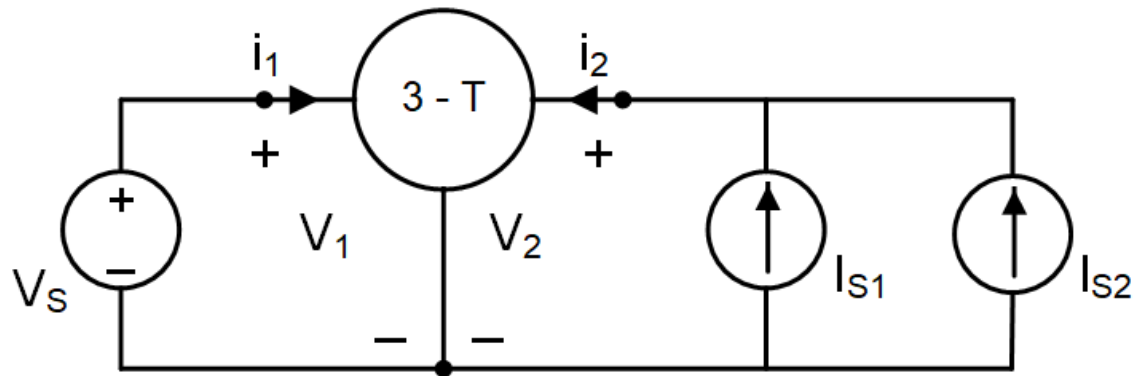
$$V_S = 5V, I_{S1} = 2A, I_{S2} = 0,03\cos(3t) A, V_2 = i_2^2 + i_1 V_1, i_1 = 0,5 V_1 - V_2$$



Deadline of the 7th HW is **25 April 2018 12:30**.