

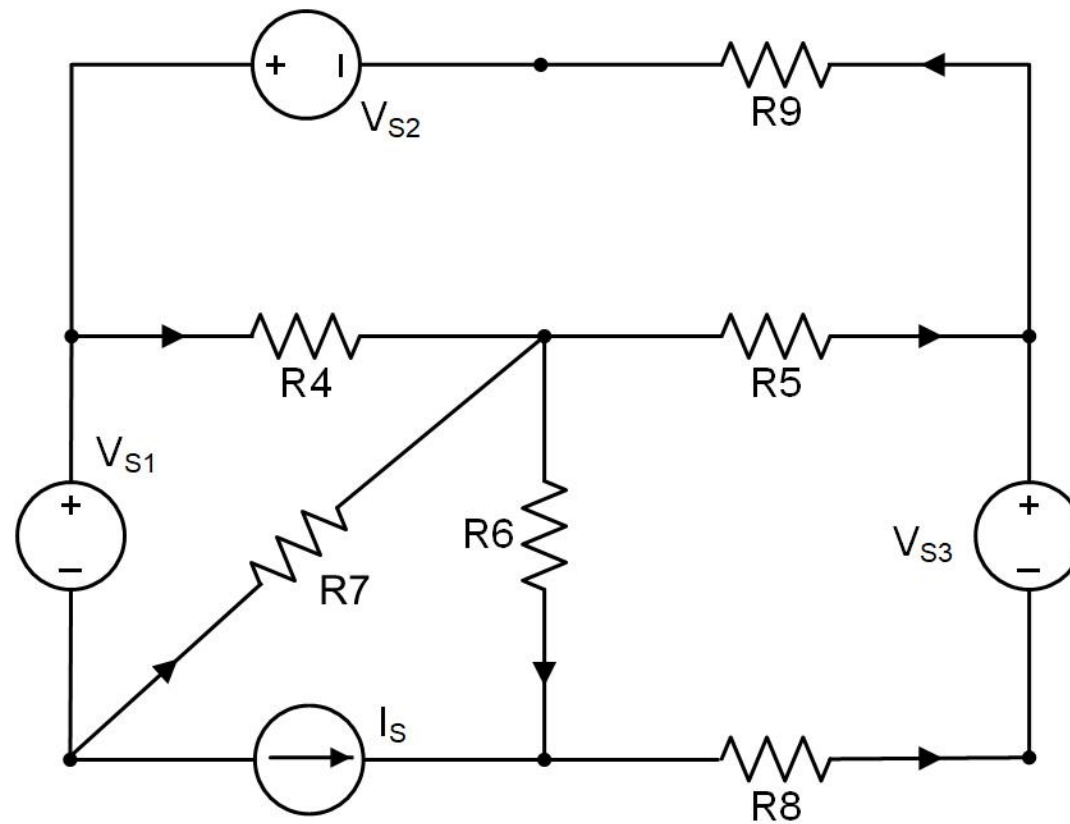
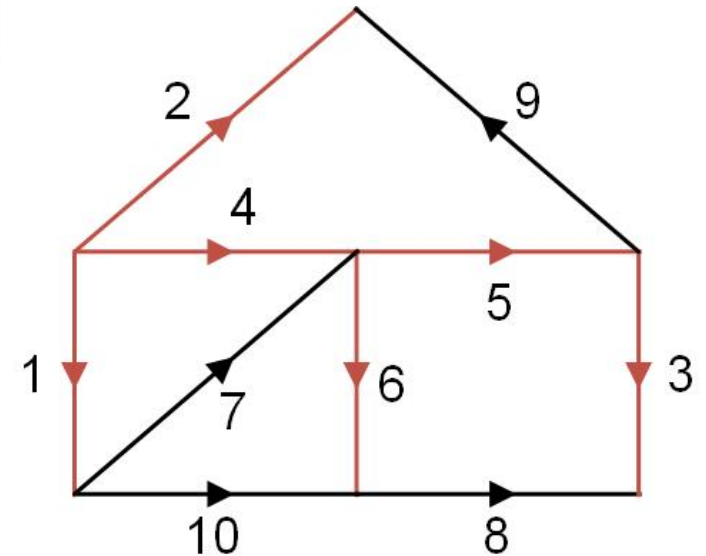


Twig Voltage Method

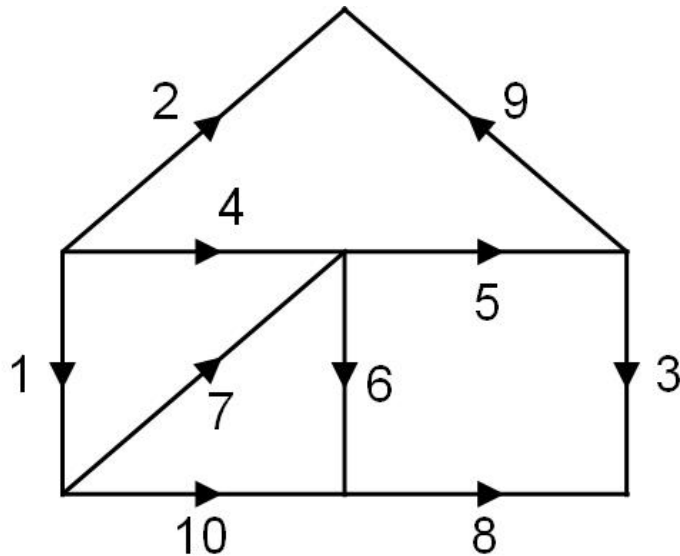

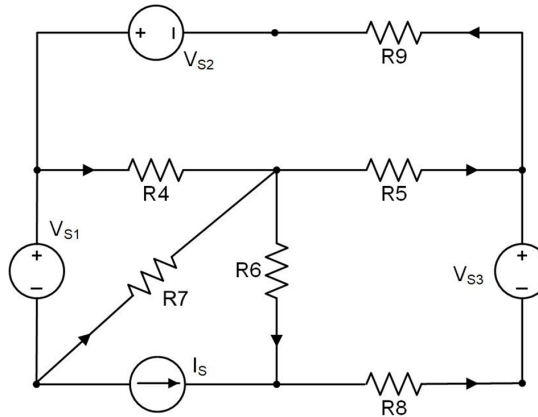1. Circuit graph is drawn. A tree is chosen: voltage source should be a twig.




2. Fundamental cut set equations are written for the twigs with unknown voltages.

4: $i_4 = \dots$

5: $i_5 = \dots$

6: $i_6 = \dots$

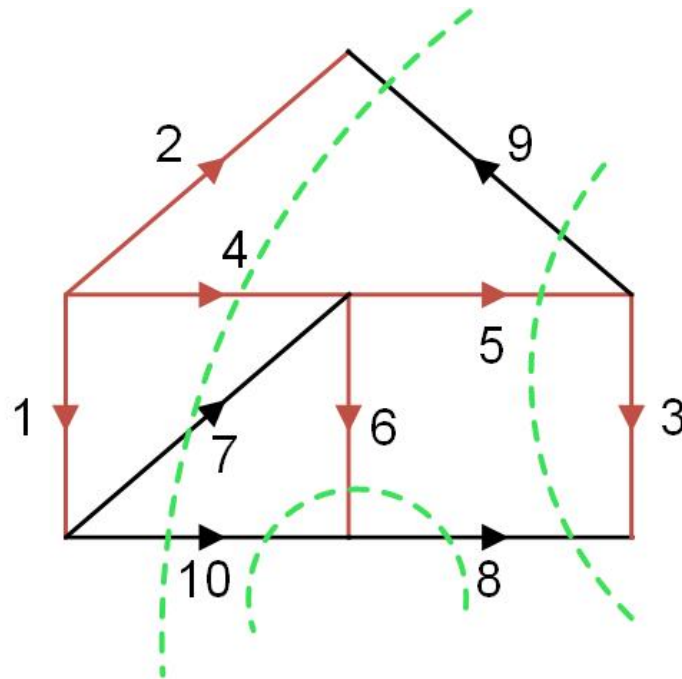

3. $i = Gv$ is inserted into the cut set equations

$$G_4 v_4 = \dots$$

$$G_5 v_5 = \dots$$

$$G_6 v_6 = \dots$$

4. Link voltages is written in terms of twig voltages using loop equations.

$$V_7 = \dots$$

$$V_8 = \dots$$

$$V_9 = \dots$$

5. Twig voltages are inserted into fundamental cut set equations

$$G_4 v_4 = \dots$$

$$G_5 v_5 = \dots$$

$$G_6 v_6 = \dots$$

6. Unknown twig voltages (v_4, v_5, v_6) are written in terms of known voltages.

$$\begin{bmatrix} G_4 + G_7 + G_9 & G_9 & 0 \\ G_9 & G_5 + G_8 + G_9 & -G_8 \\ 0 & -G_8 & G_6 + G_8 \end{bmatrix} \begin{bmatrix} V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} G_7 & G_9 & 0 & -1 \\ 0 & G_9 & -G_8 & 0 \\ 0 & 0 & G_8 & -1 \end{bmatrix} \begin{bmatrix} V_{s1} \\ V_{s2} \\ V_{s3} \\ I_s \end{bmatrix}$$

$$\mathbf{Ax} = \mathbf{Bu} \rightarrow \mathbf{x} = \mathbf{A}^{-1}\mathbf{Bu}$$

Link Current Method

1. Fundamental loop equations are written for the unknown link currents.

$$V_7 = \dots$$

$$V_8 = \dots$$


$$V_9 = \dots$$

2. $V = Ri$ is inserted into the fundamental loop equations.

$$R_7 i_7 = \dots$$

$$R_8 i_8 = \dots$$

$$R_9 i_9 = \dots$$

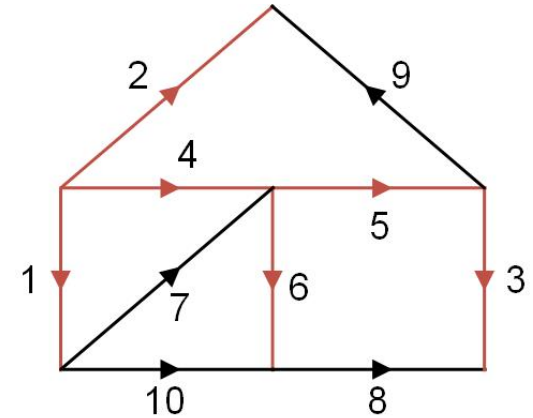

3. Twig currents are written in terms of link currents using cut set equations.

$$i_4 = \dots$$

$$i_5 = \dots$$

$$i_6 = \dots$$

4. Twig currents are inserted into the fundamental loop equations.

$$R_7 i_7 = \dots$$

$$R_8 i_8 = \dots$$

$$R_9 i_9 = \dots$$

5. Unknown link currents can be found in terms of known ones.

$$\begin{bmatrix} R_4 + R_7 & 0 & -R_4 \\ 0 & R_5 + R_6 + R_8 & -R_5 \\ -R_4 & -R_5 & R_4 + R_5 + R_9 \end{bmatrix} \begin{bmatrix} i_7 \\ i_8 \\ i_9 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & -R_4 \\ 0 & 0 & 1 & R_6 \\ 0 & 1 & 0 & R_4 \end{bmatrix} \begin{bmatrix} V_{s1} \\ V_{s2} \\ V_{s3} \\ I_s \end{bmatrix}$$