




BLG 231E Digital Circuits Take-Home Exam 4

Due Date: Thursday, November 21, 2019 @ 16:00 PM


- Please be diligent and show all work.
- Show complement signs by inserting a dash over the character such as: \bar{X}
- **Consequences of plagiarism:** Any cheating will be subject to the university disciplinary proceedings.
- Late submissions will **NOT** be accepted.
 - **Submissions:** Please submit your solutions to the Digital Circuits Course Assignment Box.

In this exam, you need to design a combinational circuit that performs ADD and SUBTRACT operations on 5-bit binary signed integers that are given **in sign-magnitude format** (different than 2's complement representation). In sign-magnitude format, the first bit represents the sign (0: positive, 1: negative) and the remaining bits represent the absolute value (magnitude) of the number. For example; 5-bit $+5_{10} = 0\ 0101$ and $-5_{10} = 1\ 0101$. The block diagram of the circuit is shown below. A and B are 5-bit signed numbers **in sign-magnitude format** (A4 and B4 for the signed bits and other 4 bits for the magnitudes). Result R is also in sign-magnitude format.

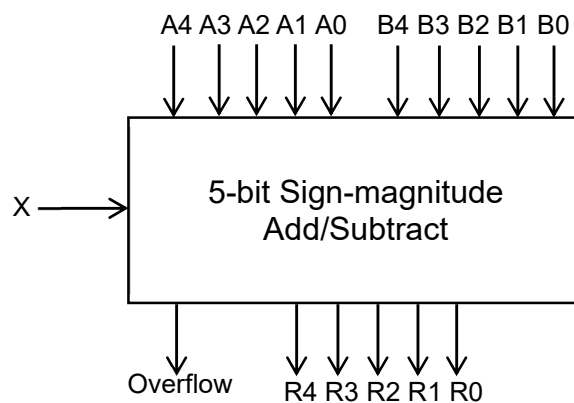If there is an overflow (the result cannot be represented in 5-bit sign-magnitude format) then the Overflow output should be 1. The input X is used to control the operation of the circuit ($X=0$: Add, $X=1$: Subtract).



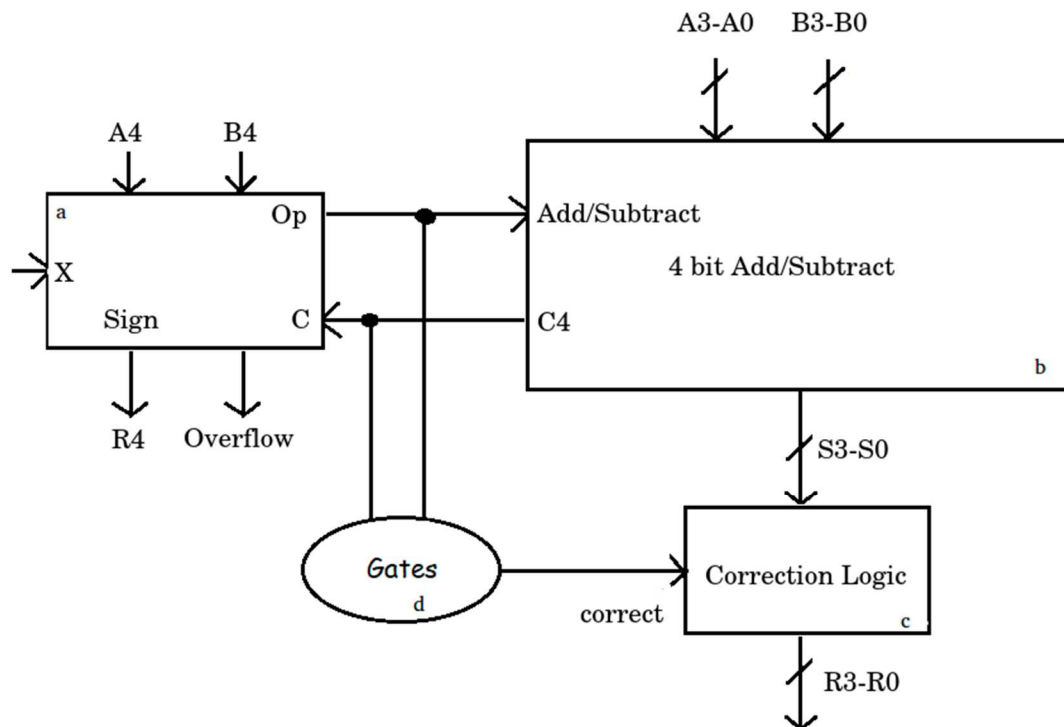You must design your circuit so that it consists of 4 subcircuits (a, b, c, and d) as explained below.



X is the operation that we wanted to do. If $X = 0$, it is addition; if $X=1$, it is subtraction.

Op is the real operator that the circuit b (2's complement adder/subtractor) will do. If $Op=0$, it is addition; if $Op = 1$, it is subtraction.

Circuit a: It determines the operator (Op) (Add or Subtract) input for the Circuit b and generates the sign of the result R based on its input values. It also generates the Overflow output.

Circuit b: It is a 4-bit parallel 2's complement Adder-Subtractor (as shown in the lecture).

Circuit c: This circuit converts the result (S3-S0) from Circuit b in 2's complement form to sign-magnitude format to obtain R3-R0 (if needed).

Circuit d: This circuit determines whether it is necessary or not to convert (S3-S0) from 2's complement form to sign-magnitude form (Correct=0 not necessary; Correct=1: necessary).

Examples:

- $A = 00101 (+5)$ $B = 10111 (-7)$ $X = 0$ (Addition)

Circuit a: $Op = 1$ (subtraction, because the required operation is addition and one of the numbers is negative)

Circuit b: $A-B$; $5-7 = 0101-0111 = 1110$; $S=1110$ $C4=0$.

Circuit a: Because after subtraction $C=0$ (no carry means borrow), $B>A$ so Sign is $R4=1$, Overflow=0.

Circuit d: Correct=1 correction is necessary.

Circuit c: Convert $S=1110$ to $R3-R0 = 0010$

Result = $R4-R0 = 10010 (-2)$

- $A = 00101 (+5)$ $B = 10111 (-7)$ $X = 1$ (Subtraction)

Circuit a: $Op = 0$ (addition, because the required operation is subtraction and one of the numbers is negative)

Circuit b: $A+B$; $5+7 = 0101+0111 = 1100$; $S=1100$ $C4=0$.

Circuit a: Sign is $R4=0$, $Overflow=0$.

Circuit d: $Correct=0$ correction is not necessary.

Circuit c: Do not convert. $R3-R0 = 1100$

Result = $R4-R0=01110 (+12)$

- $A = 01000 (+8)$ $B = 01001 (+9)$ $X = 1$ (Subtraction)

Circuit a: $Op = 0$ (Subtraction, because the required operation is subtraction and both numbers are positive)

Circuit b: $A-B$; $8-9 = 1000-1001 = 1111$; $S=1111$ $C4=0$.

Circuit a: Because after subtraction $C=0$ (no carry means borrow), $B>A$ so Sign is $R4=1$, $Overflow=0$.

Circuit d: $Correct=1$ correction is necessary.

Circuit c: Convert $S=1111$ to $R3-R0 = 0001$

Result = $R4-R0=10001 (-1)$

- $A = 01000 (+8)$ $B = 01001 (+9)$ $X = 0$ (Addition)

Circuit a: $Op = 0$ (addition, because the required operation is addition and both numbers are positive)

Circuit b: $A+B$; $8+9 = 1000+1001 = 0001$; $S=0001$ $C4=1$.

Circuit a: Sign is $R4=\Phi$ (don't care), $Overflow=1$. There is a carry after addition; this value cannot be represented in a 5-bit sign-magnitude format.

Circuit d: $Correct=\Phi$ (don't care).

Circuit c: $R3-R0 = \Phi$ (don't care).

a) Draw the truth table for the Circuit a.

Write the simplest expression for the outputs Op , $Sign$, and $Overflow$.

Draw the circuit using any type of logic gates.

Fully label all input and outputs.

b) Design and draw the Circuit c using only half adders and minimum number of logic gates. Fully label all input and outputs.

c) Design and draw the Circuit d using any type of logic gates.

Fully label all input and outputs.