



## BLG 231E - Digital Circuits

### Assignment 5

**Due Date:** 19.12.2019, Thursday, 16:00.

- Please **write and draw neatly** and prepare your homework on computer.
  - Show complement signs by inserting a dash over the character such as:  $\bar{x}$
  - **Consequences of plagiarism:** Any cheating will be subject to the University disciplinary proceedings.
  - **No late submissions** will be accepted.
  - **Submissions:** Please submit your solutions to the Digital Circuits Course Assignment Box.
  - If you have any question, please send e-mail to [pamay@itu.edu.tr](mailto:pamay@itu.edu.tr)
1. Analyze the synchronous sequential circuit given in the figure below by answering following questions.
    - Determine the input functions of the flip-flops.
    - Determine the next states (use  $Q_0$  for JK-FF, and  $Q_1$  for D-FF) and output expression.
    - Derive the state/output table.
    - Draw the state transition diagram.
  2. Assume that the machine is in state 00 and the output is also 0. Write the shortest possible sequence of X (consecutive values of X) that makes the output 1.

