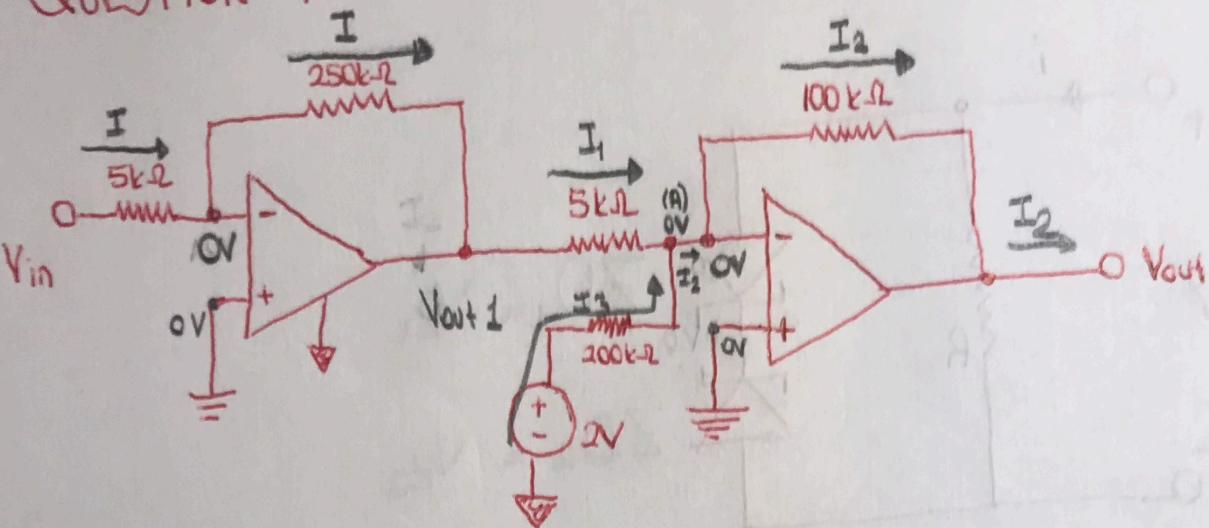


QUESTION 1:



$$V_{out} = ?$$

$$V_{out1} = -V_{in} \cdot \frac{250}{5} = -50V_{in}$$

$$I_1 + I_2 - I_3 = 0 \rightarrow \text{KCL at point A.}$$


$$\frac{V_{out1} - 0V}{5k\Omega} + \frac{2V - 0V}{200k\Omega} - \frac{0V - V_{out}}{100k\Omega} = 0$$

$$\frac{-50V_{in}}{5k\Omega} + \frac{2V}{200k\Omega} + \frac{V_{out}}{100k\Omega} = 0 \Rightarrow \frac{V_{out}}{100k\Omega} = \frac{10V_{in}}{5k\Omega} - \frac{2V}{100k\Omega}$$

So $V_{out} = 1000V_{in} - 1$

QUESTION 2:

TENFİK OZEN
150180082

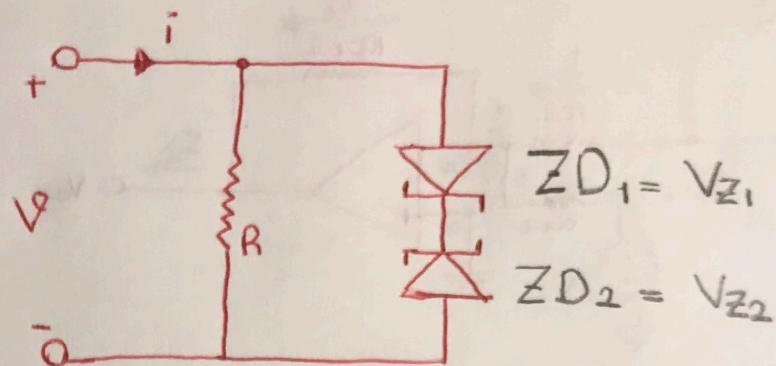


Find nonlinear i-v characteristic of circuit


If $V > 0$, first zener diode is forward biased and second zener diode is reverse biased. So until $V < V_{fb} + V_{z2}$ there won't be current. And after that point zener diodes will act like voltage regulator.

If $V < 0$, first zener diode is reverse biased and second zener diode is forward biased. So until $V > -V_{fb} - V_{z1}$ there won't be current. After that point zener diodes will act like voltage regulator.


i-v characteristic of Zener diodes:

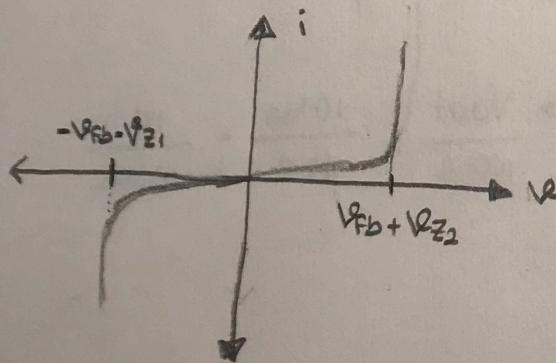


i-v characteristic of resistor

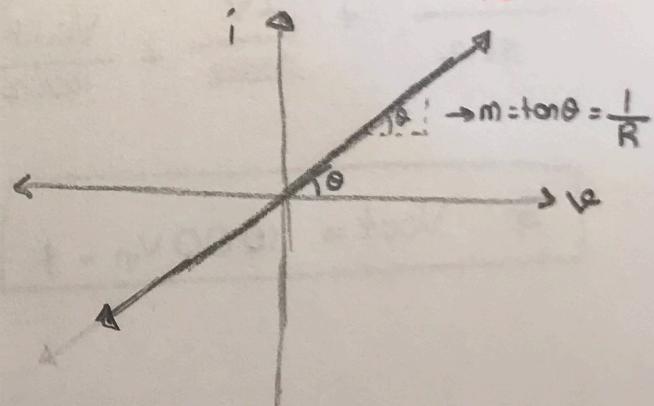

i-v characteristic of circuit:

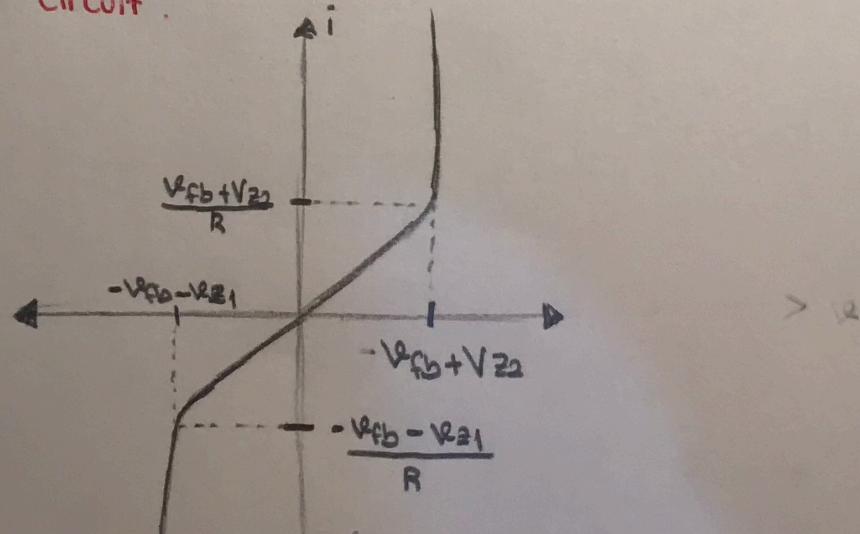

QUESTION 3:

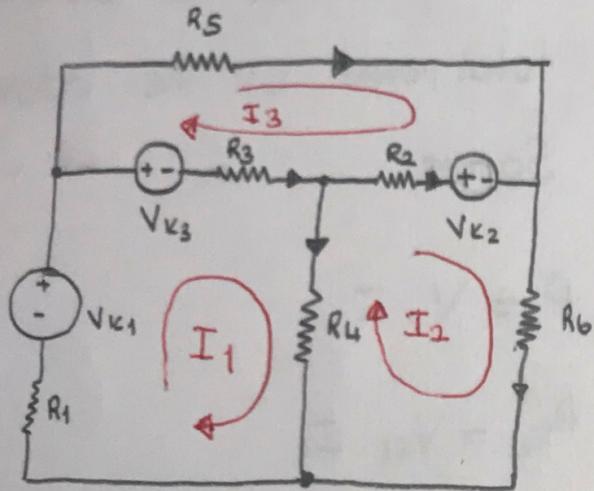

KVL at MESH 1: $I_1 R_1 - V_{k1} + V_{k3} + (I_1 - I_3) R_3 + (I_1 - I_2) R_4 = 0 \quad (1)$

KVL at MESH 2: $I_2 R_6 + (I_2 - I_1) R_4 + (I_2 - I_3) R_2 + V_{k2} = 0 \quad (2)$

KVL at MESH 3: $I_3 R_5 - V_{k2} + (I_3 - I_2) R_2 + (I_3 - I_1) R_3 - V_{k3} = 0 \quad (3)$

From Eq (1): $I_1 R_1 + I_1 R_3 - I_3 R_3 + I_1 R_4 - I_2 R_4 - V_{k1} + V_{k3} = 0$
So $(R_1 + R_3 + R_4) \cdot I_1 - R_3 \cdot I_3 - R_4 \cdot I_2 = V_{k1} - V_{k3}$

From Eq (2): $I_2 R_6 + I_2 R_4 - I_1 R_4 + I_2 R_2 - I_3 R_2 + V_{k2} = 0$
So $-R_4 \cdot I_1 - (R_6 + R_4 + R_2) \cdot I_2 + R_2 \cdot I_3 = V_{k2}$

From Eq (3): $I_3 R_5 - V_{k2} + I_3 R_2 - I_2 R_2 + I_3 R_3 - I_1 R_3 - V_{k3} = 0$
So $-I_1 R_3 - I_2 R_2 + (R_3 + R_5 + R_2) I_3 = V_{k3} + V_{k2}$

$$\begin{bmatrix} R_1 + R_3 + R_4 & -R_4 & -R_3 \\ R_4 & -(R_6 + R_4 + R_2) & R_2 \\ -R_3 & -R_2 & R_3 + R_5 + R_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_{k1} - V_{k3} \\ V_{k2} \\ V_{k3} + V_{k2} \end{bmatrix}$$

$$I_1 = \frac{\begin{vmatrix} V_{K1}-V_{K3} & -R_4 & -R_3 \\ V_{K2} & -(R_6+R_4+R_2) & R_2 \\ V_{K3}+V_{K2} & -R_2 & R_3+R_5+R_2 \end{vmatrix}}{\begin{vmatrix} R_1+R_3+R_4 & -R_4 & -R_3 \\ R_4 & -(R_6+R_4+R_2) & R_2 \\ -R_3 & -R_2 & R_3+R_5+R_2 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} R_1+R_3+R_4 & V_{K1}-V_{K3} & -R_3 \\ R_4 & V_{K2} & R_2 \\ -R_3 & V_{K3}+V_{K2} & R_2+R_3+R_5 \end{vmatrix}}{\begin{vmatrix} R_1+R_3+R_4 & -R_4 & -R_3 \\ R_4 & -(R_6+R_4+R_2) & R_2 \\ -R_3 & -R_2 & R_3+R_5+R_2 \end{vmatrix}}$$

$$I_3 = \frac{\begin{vmatrix} R_1+R_3+R_4 & -R_4 & V_{K1}-V_{K3} \\ R_4 & -(R_6+R_4+R_2) & V_{K2} \\ -R_3 & -R_2 & V_{K3}+V_{K2} \end{vmatrix}}{\begin{vmatrix} R_1+R_3+R_4 & -R_4 & -R_3 \\ R_4 & -(R_6+R_4+R_2) & R_2 \\ -R_3 & -R_2 & R_3+R_5+R_2 \end{vmatrix}}$$

Since we know I_1 , I_2 and I_3 values we can determine total power of the independent Sources.

$$P = V \cdot I$$

$$P_{V_{K1}} = V_{K1} \cdot I_1$$

$$P_{V_{K2}} = V_{K2} \cdot (I_2 - I_3)$$

$$P_{V_{K3}} = V_{K3} \cdot (I_1 - I_3)$$